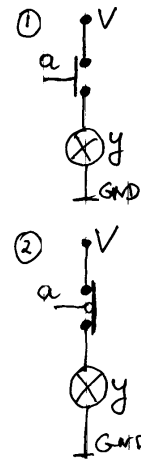


1 Introductory concepts

1.1 Switches. NOT operation

At the beginning there was THE SWITCH

- Switches come in two versions: “normally open” (1) (open when in-active) and “normally closed” (2) (closed when in-active)
- When a switch, say a , is in its neutral position, we say that $a = 0$. When a switch is activated, we say that $a = 1$,
- V indicates a supply voltage (one end of battery). **GND** indicates the ground terminal (the other end of a battery). The crossed circle symbolizes a bulb.
- The symbols $\{0, 1\}$ will be synonymously used with words like { off, on }, { false, true }, { low, high }, etc.
- If we consider a as an **input variable** (argument), and y as an **output variable** (function value) then



Truth tables:

①

y	a	y
0	0	0
1	1	1

$y = a$

②

a	y
0	1
1	0

$y = \bar{a}$
= NOT a

the first circuit (1) performs the **identity operation** (function) $y = a$ and the second circuit (2) performs the **NOT operation** (function) $y = \bar{a} = \text{NOT } a = a'$ also known as the **complement** or the **inversion operation**


1.2 Parallel connection of switches

- Two switches can be connected in parallel:
- The operation performed by the circuit can be described by the following logical expression

$$\text{if } a = 1 \text{ or } b = 1 \text{ then } y = 1 \text{ else } y = 0$$

- Alternatively, the operation can be described by the following **truth table**:
- Formally we can say that if we have **two binary variables** $a, b \in \{0, 1\}$ and the operation performed can be symbolically described as
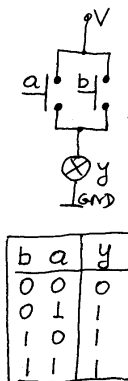
$$y = f(a, b) = a \text{ or } b = a + b$$



b	a	y
0	0	0
0	1	1
1	0	1
1	1	1

- Hence we say that the circuit performs the **or** operation, also known as a **logic sum** operation


1.3 Serial connection of switches

- Two switches can be connected serially:
- The operation performed by the circuit can be described by the following logical expression

$$\text{if } a = 1 \text{ and } b = 1 \text{ then } y = 1 \text{ else } y = 0$$

- Alternatively, the operation can be described by the following **truth table**:
- Formally we can say that if we have **two binary variables** $a, b \in \{0, 1\}$ and the operation performed can be symbolically described as
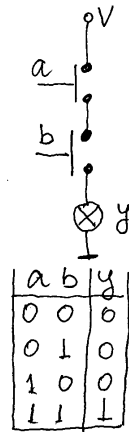
$$y = f(a, b) = a \text{ and } b = a \cdot b$$



- Hence we say that the circuit performs the **and** operation, also known as a **logic multiplication** operation

1.4 Exercise

- Consider serial-parallel connections of **three** switches, a, b, c
- Draw related **circuit diagrams** and **truth tables**.
- Describe circuits by relevant logic expressions **if** ...