 


### 3 Logic Gates and Boolean Algebra


#### 3.1 CMOS Technology

- Digital devices are predominantly manufactured in the Complementary-Metal-Oxide-Semiconductor (CMOS) technology.
- Two types of switches, as discussed in sec. 1.1, are implemented as a pair of complementary MOS Fields-Effect-Transistors FETs:

- nMOS transistor — “normally open” switch,
- pMOS transistor — “normally closed” switch,



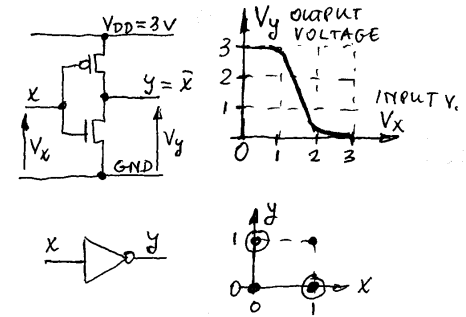- Such pair of transistors is used to build an **inverter** and consequently all digital devices
- When the input voltage  $V_x$  is **low**, that is, the logic signal  $x = 0$ , the pMOS transistor is closed and nMOS transistor is open. Consequently the output voltage  $V_y$  is **high**, that is, the logic signal  $y = 1$ .
- The inverse situation occurs when the input voltage is **high**.



#### 3.2 Boolean Algebra and Logic Gates

Operations performed by logic gates can be conveniently described in Boolean algebra. The (two-valued) Boolean algebra is defined on


- a set of two elements,  $\mathcal{B} = \{0, 1\}$ ,
- two binary operators, OR (+) and AND ( $\cdot$ ),
- one unary operator, NOT ( $'$ ), ( $\bar{\phantom{x}}$ )

Two Boolean values 0 and 1 correspond to

- two values, “false” and “true” used in mathematical logic, and to
- two voltage levels, “LOW” and “HIGH” used in switching circuits.

 **Three basic Boolean (logic) operations**

name:      AND                  OR                  NOT



operation:  $y = x_1 \cdot x_0$      $y = x_1 + x_0$      $y = x_1'$

$x_1$	$x_0$
0	0
0	1
1	0
1	1

$y$
0
0
0
1

$y$
0
1
1
1

$y$
1
0

A 2-variable **truth table** lists values of the output signal  $y \in \{0, 1\}$  (results of logic operations) for all possible combinations of input signals,  $x_1, x_0 \in \{0, 1\}$  (operands).

- The result of the **AND operation** is 1 if and only if both operands are 1.

We also say that the output of the AND gate is HIGH (asserted) if both input signals are HIGH (asserted).


- The AND operation or **logic multiplication** is identical with arithmetic multiplication.
- The result of the **OR operation** is 1 if at least one operand is 1.

We also say that the output of the OR gate is HIGH (asserted) if at least one input signal is HIGH (asserted).

- The OR operation or **logic addition** differs from arithmetic addition, because  $1 + 1 = 1$  not 2!
- The **NOT operator** or logic complement can be arithmetically interpreted by the following expression:  $x' = 1 - x$
- The NOT gate or **INVERTER** complements input signals:  $0' = 1, 1' = 0$ .

 **3.3 Timing diagrams**

Operations performed by logic gates can also be described by means of timing diagrams.



In the example the pair of input signals  $x_1, x_0$  goes through all possible combinations in the following way:

$$x = (x_1x_0)_2 \in \{0, 1, 3, 2\}$$

Such a code is known as the Gray code

### 3.4 Boolean Expressions and Logic Diagrams

Boolean expressions are formed from:

- two Boolean constants, (0, 1),
- three basic logic operations, ( $\cdot$ ,  $+$ ,  $'$ ), and
- parentheses ( ).

The order of evaluation is:


- expressions inside parentheses,
- complement (NOT),
- logic multiplication (AND),
- Logic addition (OR).

Consider a Boolean (logic) expression

$$f = a + b' \cdot c = a + \bar{b} \cdot c$$

where  $a, b, c, f$  and Boolean variables.


The equivalent logic diagram:

 

In order for the logic addition to be performed before multiplication we have to add parentheses:

$$f = (a + b') \cdot c = (a + \bar{b}) \cdot c$$

The equivalent logic diagram:

 

The AND operator (the multiplication sign) may be omitted and we can write

$$f = a + b'c \text{ or } f = (a + b')c$$

Identify:

- input-output ports, or signals (wires) connected to the outside world
- gates and
- signal or nets (wires), that is. signals interconnecting gates inputs and outputs.

### 3.5 VHDL Hardware Description Language — example 1

- Digital devices/circuits can be described/modelled using a hardware description language, VHDL.
- The description consists of two main parts:
- **Input-output ports** are specified by the **ENTITY**
- The **circuit structure or function** is specified by an **ARCHITECTURE**

#### Example:

- The contents of the **log\_circ\_1.vhd** file:

```
-- this is a comment
-- VHDL is NOT case sensitive
-- To emphasize, the key words are capitalized
-- this is a black-box a logic circuit

ENTITY log_circ_1 IS
  PORT (a, b, c : IN BIT ;
        f      : out BIT ) ;
END [ENTITY] log_circ_1 ;

-- an architecture for log_circ_1

ARCHITECTURE arch_1 OF log_circ_1 IS

BEGIN
  f <= ( a OR NOT b) AND c ; -- a SIGNAL assignment
END [ARCHITECTURE] arch_1 ;
```

### 3.6 Truth tables and Karnaugh Maps

The behaviour of a logic circuit, that is, the values of the output signals for all combinations of input signals can be equivalently described by:

- a Boolean expression,
- the truth table,
- the Karnaugh map,

Consider the following Boolean (logic Function

$$f = (a' + b)c$$

The **truth table** lists the values of the function  $f$  for all  $2^3 = 8$  combinations of three input variables

$(cba)_2$	$c$	$b$	$a$	$a'$	$a' + b$	$f$
0	0	0	0	1	1	0
1	0	0	1	0	0	0
2	0	1	0	1	1	0
3	0	1	1	0	1	0
4	1	0	0	1	1	1
5	1	0	1	0	0	0
6	1	1	0	1	1	1
7	1	1	1	0	1	1

### 3.7 A 3-variable Karnaugh map

- Karnaugh maps are representations of Boolean hyper-cubes.

A concept of adjacent vertices

A Karnaugh map for


$$f = (a' + b)c$$

$\begin{matrix} b & a \\ c \end{matrix}$	00	01	11	10
0	0	0	0	0
1	1	0	1	1
 
### 3.8 Theorems of Boolean Algebra and their circuit interpretation


Transformations and simplification of logic circuits are based on a variety of Boolean algebra theorems which can easily be verified by

- Double Complement — Involution property




Double NOT operation can be removed.

- Operations with constants

 

- Operations with repeated arguments

 

- OR and AND are commutative operations — all gate inputs are identical:


$$\text{OR: } a + b = b + a \quad \text{AND: } a \cdot b = b \cdot a$$

- OR and AND are associative operations —  $n$ -input gates exist:

$$\text{OR: } a + (b + c) = (a + b) + c = a + b + c$$


- OR operation (logic addition) is distributive
 
$$a \cdot (b + c) = a \cdot b + a \cdot c$$



- AND operation (logic multiplication) is **also** distributive!
 
$$a + b \cdot c = (a + b) \cdot (a + c)$$



Verification of the distributive law for the AND operation using the truth table method:

$$a + b \cdot c = (a + b) \cdot (a + c)$$

$(cba)_2$	$c$	$b$	$a$	$b \cdot c$	LHS	$a + b$	$a + c$	RHS
0	0	0	0	0	0	0	0	0
1	0	0	1	0	1	1	1	1
2	0	1	0	0	0	1	0	0
3	0	1	1	0	1	1	1	1
4	1	0	0	0	0	0	1	0
5	1	0	1	0	1	1	1	1
6	1	1	0	1	1	1	1	1
7	1	1	1	1	1	1	1	1

For all combinations of variables  $LHS = RHS$ , therefore, the distributive law for the logic multiplication is valid.

### Duality Principle

Every theorem of the Boolean algebra remains valid if the **operators** and **constants** are interchanged, that is:

$$\begin{aligned} \text{AND} &\iff \text{OR} \\ 1 &\iff 0 \end{aligned}$$

#### Example:

If the following equality

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

is valid, then interchanging '+' with '·' we obtain the **dual** equality:

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

which is also valid.

### Absorption Rules

1.  $a + a \cdot b = a$

Verification by algebraic manipulation:

$$a + a \cdot b = a \cdot (1 + b) = a, \text{ because } 1 + b = 1$$

2.  $a \cdot (a + b) = a$  — the dual equality

3.  $a + a' \cdot b = a + b$  — Important!


4.  $a \cdot (a' + b) = a \cdot b$

Absorption rules are important in circuit simplification.

**De Morgan's Theorems**

1. The complement of a product (AND) is equal to the sum (OR) of the complements:

$$(a \cdot b)' = a' + b'$$

 


equivalently




**This is the NAND gate (NOT AND)**

2. The complement of a sum (OR) is equal to the product (AND) of the complements (the dual theorem):

$$(a + b)' = a' \cdot b'$$

 

equivalently

 

**This is the NOR gate (NOT OR)**

**3.9 All two-variable functions**  $y = F(b, a)$

b	0	0	1	1	
a	0	1	0	1	
$F_0$	0	0	0	0	0
$F_1$	0	0	0	1	$b \cdot a$ AND $\Rightarrow$
$F_2$	0	0	1	0	$b \cdot \bar{a}$
$F_3$	0	0	1	1	b
$F_4$	0	1	0	0	$\bar{b} \cdot a$
$F_5$	0	1	0	1	a
$F_6$	0	1	1	0	$\bar{b} \cdot a + b \cdot \bar{a} = b \oplus a$ XOR $\Rightarrow$
$F_7$	0	1	1	1	$b + a$ OR $\Rightarrow$
$F_8$	1	0	0	0	$(\overline{b+a}) = \bar{b} \cdot \bar{a}$ NOR $\Rightarrow$
$F_9$	1	0	0	1	$\bar{b} \cdot \bar{a} + b \cdot a = (\overline{b \oplus a})$ XNOR $\Rightarrow$
$F_{10}$	1	0	1	0	$\bar{a}$
$F_{11}$	1	0	1	1	$b + \bar{a}$
$F_{12}$	1	1	0	0	$\bar{b}$
$F_{13}$	1	1	0	1	$\bar{b} + a$
$F_{14}$	1	1	1	0	$\bar{b} \cdot \bar{a} = \overline{b+a}$ NAND $\Rightarrow$
$F_{15}$	1	1	1	1	1



### 3.10 NAND and NOR gates

the truth tables for the NAND and NOR gates

$x_1, x_2$	$\overline{x_1 x_2}$ $= \overline{x_1} + \overline{x_2}$	$\overline{x_1 + x_2}$ $= \overline{x_1} \cdot \overline{x_2}$
00	1	1
01	1	0
10	1	0
11	0	0
	NAND	NOR

Alternative, functional description of  
NAND and NOR gates

