 


## 6 Combinational circuits

### 6.1 Introductory concepts

- A combinational circuit (block, component) consists of logic gates and processes  $n$  input signals  $x(n-1), \dots, x(0)$  into  $m$  output signals  $y(m-1), \dots, y(0)$  using a function  $y = f(x)$ , in such a way that output signals depend only on the **current** input signals.




where each  $f_i$  is a logic function.


- Past values of the input signals do not have any influence on the current values of the output signals.
- Description of any combinational circuit with  $n$  inputs and  $m$  outputs can be ultimately reduced to a **truth table** with  $2^n$  rows and  $m$  column.
- From the point of view of their internal structures combinational blocks can be classified into two groups:
  - un-structured circuits, that is a “random” collection of gates,
  - structured circuits forming 1-D and 2-D arrays of components.

- The simplest combinational blocks are collections of gates.

For example, an  $n$ -bit NAND gate:

 

 - A slightly more complicated example includes the collection of gates driven by a common **control signal**, say  $s$ , to perform two operations:




Function/operation Table:

$s$	function
0	$y(1:n) = a(1:n)$
1	$y(1:n) = \bar{a}(1:n)$

- We are already familiar with a  $n$ -to- $2^n$  **decoder** as a minterm/maxterm generator. Typically the decoder has an additional **enable signal**  $s$  such that the minterms are generated only for  $s=1$ , whereas for  $s=0$  outputs are in an inactive state, typically 0.


$s$	$x_1$	$x_0$	$m_0$	$m_1$	$m_2$	$m_3$
0	—	—	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

Function/operation Table:

$x$	$y_0$	$y_1$	$y_2$	$y_3$
0	$s$	0	0	0
1	0	$s$	0	0
2	0	0	$s$	0
3	0	0	0	$s$

 - The decoder can be also used as a **Demultiplexer**. The 1-bit demultiplexer receives 1-bit data on a single input and re-directs it into one-out-of  $m = 2^n - 1$  outputs selected by an  $n$ -bit number  $x$



### 6.2 Example of a VHDL code for a 2-to-4 decoder

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY dec2to4 IS
  PORT (
    x : IN      std_logic_vector (1 DOWNT0 0);
    y : OUT     std_logic_vector (3 DOWNT0 0)
  );
END dec2to4 ;

ARCHITECTURE struct OF dec2to4 IS
  SIGNAL xb : std_logic_vector(1 DOWNT0 0);
BEGIN
  y(0) <= xb(1) AND xb(0);
  y(1) <= xb(1) AND x(0);
  y(2) <= xb(0) AND x(1);
  y(3) <= x(1)  AND x(0);
  xb  <= NOT(x);
END struct;


```

- A VHDL program represents a digital circuit.
- It can represent: **signal flow, behaviour or structure** of the circuit
- The program can be used to simulation/test, or to synthesize the digital circuit
- The above program describes **signal flow**
- All assignment statements are interpreted/executed **concurrently**, therefore can be written in **any order**.

 
### 6.3 Multiplexers

- A **n-to-1 multiplexer** connects its output  $y$  to one of  $n = 2^m$  inputs  $a_0, a_1, \dots, a_n$  selected by an  $m$ -bit control/select signal  $s$ .
- In other words the multiplexer output is a sum of products of input signals with respective minterms:


$$y = a_0 \cdot m_0 + a_1 \cdot m_1 + \dots + a_{n-1} \cdot m_{n-1} = \sum_{i=0}^{n-1} a_i \cdot m_i$$



 - A 4-to-1 multiplexer can be implemented in the following way:




Function Table:

 
 
### 6.4 Describing a multiplexer in VHDL

There are a number of ways to describe a multiplexer in VHDL. The following two methods use various concurrent assignment statements. We use a 4-to-1 multiplexer as an example.



```
ENTITY mux4to1A IS
  PORT (a : IN std_logic_vector (0 to 3) ;
        s : IN std_logic_vector (1 downto 0) ;
        y : OUT std_logic ) ;
END mux4to1A ;
```

#### 6.4.1 Conditional Signal Assignment Statement

`<= ... when ... else`

```
ARCHITECTURE condSA OF mux4to1A IS
  BEGIN
    y <= a(0) WHEN s = "00" ELSE
      a(1) WHEN s = "01" ELSE
      a(2) WHEN s = "10" ELSE
      a(3) ;
  END condSA ;
```

#### 6.4.2 Selected Signal Assignment Statement


`<= with ... select ... when ... , ... ;`

```
ARCHITECTURE selSA OF mux4to1A IS
  BEGIN
    WITH s SELECT
      y <= a(0) WHEN "00" , -- comma
      a(1) WHEN "01" ,
      a(2) WHEN "10" ,
      a(3) WHEN OTHERS ; -- semicolon
  END selSA ;
```
 
### Multiplexer as a universal logic element

- Typically multiplexers are used to re-direct signals from different sources onto a common output.
- However, when we compare expression for canonical implementation of a logic function with expression for a multiplexer we note that they are structurally identical.
- It means that a multiplexer with  $m$  select signals can be used as a universal logic block implementing any logic function of  $m$  variables specified by constants (from a truth table) at the multiplexer inputs.
- As an example consider implementation of a 3-variable function using an 8-to-1 multiplexer:

$$y = f(x_2, x_1, x_0) = \sum(1, 3, 5, 6)$$



- If we allow inputs to the multiplexer to be not only constants (0, 1), but also variable(s) (or their complements), then, in particular, using a  $2^m$ -to-1 multiplexer, we can implement any logic function of  $m + 1$  variables.
- In such a case  $m$  variables are applied to the select inputs of the multiplexer, whereas the remaining variable, its complement and constants (0, 1) are applied to the multiplexed inputs.

**Example**

Implement a 3-variable function


$$y = f(x_2, x_1, x_0) = \sum(1, 3, 4, 5)$$

using a  $2^2$ -to-1 multiplexer

• TRUTH TABLE

$x_{2:0}$	$x_2$	$x_1$	$x_0$	$y$	
0	0	0	0	1	$m_0$
1	0	0	1	0	$m_1$
2	0	1	0	1	$m_2$
3	0	1	1	0	$m_3$
4	1	0	0	1	$m_4$
5	1	0	1	1	$m_5$
6	1	1	0	0	$m_6$
7	1	1	1	0	$m_7$

Connect  $x_1, x_0$  to the select lines

 


- Variables  $(x_1, x_0)$  are used as the select variables in a 4-to-1 multiplexer
- The remaining variable  $x_2$  will be used at the multiplexer inputs.

• MODIFIED TRUTH TABLE

$x_{1:0}$	$x_1$	$x_0$	$y$	
0	0	0	1	$m'_0$
1	0	1	$x_2$	$m'_1$
2	1	0	$\bar{x}_2$	$m'_2$
3	1	1	0	$m'_3$

 
$$y = m_0 + m_2 + m_4 + m_5 = m'_0 \cdot 1 + m'_1 \cdot x_2 + m'_2 \cdot \bar{x}_2 + m'_3 \cdot 0$$




- To do this we modify the truth table comparing values of the output signal  $y$  for two values of the variable  $x_2$

 **6.5 Unstructured combinational circuits**

- The name “unstructured” refers to implementations of a  $n$ -input  $m$ -output combinational circuit build from simple gates which are not grouped into any sub-blocks.
- To illustrate the concept let us consider the following implementation of a **2-bit multiplier**.
- It is a 2-bit by 2-bit multiplication circuit that forms a 4-bit product:



 $a = (a_1, a_0)_2$  is a 2-bit MULTIPlicAND  
 $b = (b_1, b_0)_2$  is a 2-bit MULTIPLIER  
 $c = (c_3, c_2, c_1, c_0)_2$  is a 4-bit product  
 such that  $\boxed{c = a \cdot b} = f(a, b)$



4 Boolean functions of 4 variables must be derived

$$c_3 = f_3(a_1, a_0, b_1, b_0)$$

$$c_2 = f_2(a_1, a_0, b_1, b_0)$$

$$c_1 = f_1(a_1, a_0, b_1, b_0)$$

$$c_0 = f_0(a_1, a_0, b_1, b_0)$$

FUNCTION TABLE			TRUTH TABLE								
$a$	$b$	$C$	$a_1$	$a_0$	$b_1$	$b_0$	$m$	$c_3$	$c_2$	$c_1$	$c_0$
0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	1	0	0	1	0	0	0	0
0	2	0	0	1	1	0	2	0	0	0	0
0	3	0	0	1	1	1	3	0	0	0	0
1	0	0	1	0	0	0	4	0	0	0	0
1	1	0	1	0	1	0	5	0	0	0	0
1	2	0	1	0	1	1	6	0	0	0	0
1	3	0	1	0	1	1	7	0	0	0	0
1	0	1	1	0	0	0	8	0	0	1	0
1	1	1	1	0	1	0	9	0	0	1	0
1	2	1	1	0	1	1	A	0	0	1	0
1	3	1	1	0	1	1	B	0	0	1	0
1	0	0	1	1	0	0	C	0	1	0	0
1	1	0	1	1	1	0	D	0	1	0	0
1	2	0	1	1	1	1	E	0	1	0	0
1	3	0	1	1	1	1	F	0	1	0	0


The next step is to convert the truth table into the Karnaugh maps:

Multiplication table:

$a_1 a_0 \backslash b_1 b_0$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	8	9	F	E
10	0	2	6	4

$C = (C_3 C_2 C_1 C_0)_2$

Individual K-maps:

 

From the Karnaugh maps we can obtain the following SoP expressions:

$$C_3 = a_1 a_0 b_1 b_0$$

$$C_2 = a_1 b_1 \bar{b}_0 + b_1 a_1 \bar{a}_0 = a_1 b_1 (\bar{a}_0 + \bar{b}_0)$$

$$C_1 = a_1 \bar{b}_1 b_0 + a_1 \bar{a}_0 b_0 + b_1 \bar{a}_1 a_0 + b_1 \bar{b}_0 a_0$$

$$= a_1 b_0 (\bar{b}_1 + \bar{a}_0) + b_1 a_0 (\bar{a}_1 + \bar{b}_0)$$

$$C_0 = b_0 a_0$$

A possible implementation with “mixed” gates: AND, OR NAND

Note that equation for  $c_1$  has been simplified so that it is no longer a standard form but a 3-level implementation:


$$C_3 = a_1 a_0 b_1 b_0$$

$$C_2 = a_1 b_1 \bar{b}_0 + b_1 a_1 \bar{a}_0 = a_1 b_1 (\bar{a}_0 + \bar{b}_0)$$

$$C_1 = a_1 \bar{b}_1 b_0 + a_1 \bar{a}_0 b_0 + b_1 \bar{a}_1 a_0 + b_1 \bar{b}_0 a_0$$

$$= a_1 b_0 (\bar{b}_1 + \bar{a}_0) + b_1 a_0 (\bar{a}_1 + \bar{b}_0)$$

$$C_0 = b_0 a_0$$

 

The above implementation is an example of an unstructured combinational circuit.