

7 Arithmetic combinational circuits

7.1 Introductory concepts

- Arithmetic combinational circuits are the most typical example of **structured or array** combinational circuits
- Typically an n -bit arithmetic circuit can be decomposed into n 1-bit circuits connected in an appropriate way.
- Most typical example is an n -bit adder that can be thought of as a 1-dimensional array of 1-bit adders.
- Examples of arithmetic circuits that form 2-dimensional arrays of 1-bit cells include fast multiplication circuits and vector rotators.
- Even simple arithmetic circuits cannot be implemented in an unstructured way:
Consider a 16-bit adder adding two 16-bit numbers.
It is equivalent to a combinational circuit with 32 inputs and 16 outputs.
The truth table of such a circuit has $2^{32} = 4,294,967,296$ rows and 16 columns.
- Unstructured implementation of such a big circuit is rather impossible.

7.2 An Incrementer

- An incrementer performs operation $y \leq a + 1$ which can be implemented as a 1-dimensional array of 1-bit incrementers
- A **1-bit incrementer** has a 1-bit input a and an **input carry** c , and generate 1-bit output y and an **output carry** d .
- The signals are related by the following arithmetic equation

$$2 \cdot d + y = a + c \quad \text{or} \quad \frac{a + c}{2} = d + \frac{y}{2}$$

- It says that the result of 1-bit incrementation, y , and an output carry d are remainder and the quotient, respectively, from division of $a + c$ by 2.
- The truth table can now be easily created.


Truth table:

1	1	2	1
c	a	d	y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- From the truth table it is easy to write equations for the output signal y and the output carry d :

$$y = a \oplus c, \quad d = a \cdot c$$

 The equations can be implemented as follows:



- The presence of the XOR gate is characteristic to all arithmetic circuits.

An n-bit Incrementer

- In order to obtain an n -bit incrementer, we arrange n 1-bit incrementers in a 1-D array, connecting their output carry ports to respective input carry ports.
- If A and Y are numbers represented by the n -bit binary words, $a(n - 1 : 0)$ and $y(n - 1 : 0)$, respectively, then the n -bit incrementer performs the operation


$$2^n d + Y = A + c_0$$

where

$d = c_n$ is the 1-bit output carry, and c_0 is the 1-bit input carry.

- Note that when $c_0 = 0$ then $Y = A$, that is, no increment is performed.
- Note also that the output carry $c_n = 1$ **if and only if** all a_i and c_0 are 1.

A 4-bit incrementer

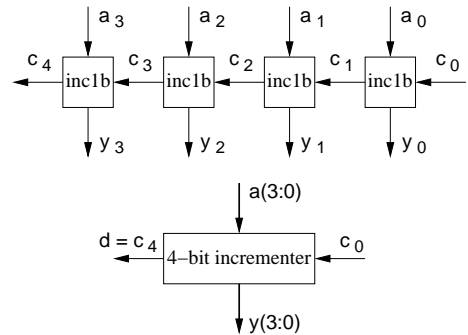

$$c_4 = \underbrace{1 \ 1 \ 1 \ 1}_{= a(3:0)} + \underbrace{1}_{= c_0} = c_0$$

$$0 \ 0 \ 0 \ 0$$

7.3 Adders

7.3.1 1-bit adder

- Adders are fundamental building blocks of all arithmetic circuits.
- Following considerations of the previous section we conclude that an n -bit adder can be built using an array of 1-bit adders.
- A **1-bit adder** has three inputs, a, b, c , and two outputs, d, s , known as the **output carry** and the **sum**, respectively.
- The 1-bit adder counts the number of ones at its three inputs and represents the result as a two-bit binary number.
- Hence, the defining arithmetic relationship between inputs and outputs can be written as:


$$a + b + c = (d, s)_2 = 2 \cdot d + s \quad \text{or} \quad \frac{a + b + c}{2} = d + \frac{s}{2}$$

- All three inputs are equivalent, but normally c is called the input carry.
- The **arithmetic equation** can be converted into a **truth table** which describes the relationship between three adder inputs c, b, a and two adder outputs, d, s , and then into the **logic equations**:

$$s = a \oplus b \oplus c$$

$$d = a \cdot b + b \cdot c + c \cdot a$$

A 1-bit adder:

 

Truth table:

c	b	a	1's	d	s
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	2	1	0
1	0	0	1	0	1
1	0	1	2	1	0
1	1	0	2	1	0
1	1	1	3	1	1

1-bit adder

Karnaugh Maps:

$$d = \sum(3, 5, 6, 7)$$


	\overline{a}			
	0	0	1	0
c	0	1	1	1
	\overline{b}			

Logic equations:

$$d = a \cdot b + b \cdot c + a \cdot c$$

$$= a \cdot b + c \cdot (a + b)$$

Generic implementation:

 

$$s = \sum(1, 2, 4, 7)$$

	\overline{a}			
	0	1	0	1
c	1	0	1	0
	\overline{b}			

$$s = \bar{c} \cdot a \cdot \bar{b} + \bar{c} \cdot \bar{a} \cdot b + c \cdot \bar{a} \cdot \bar{b} + c \cdot a \cdot b$$

$$= \bar{c} \cdot (a \cdot \bar{b} + \bar{a} \cdot b) + c \cdot (\bar{a} \cdot \bar{b} + a \cdot b)$$


$$= \bar{c} \cdot (a \oplus b) + c \cdot (\overline{a \oplus b})$$

$$= a \oplus b \oplus c$$



 7.3.2 An n-bit adder

- An n-bit adder adds two n-bit binary numbers $a = (a_{n-1} \dots a_0)$ and $b = (b_{n-1} \dots b_0)$ and a 1-bit input carry c_0 and produces an n-bit sum $s = (s_{n-1} \dots s_0)$ and a 1-bit output carry d .
- This can be formally described in the following way:




$$s = a + b + c_0 = \sum_{i=0}^{n-1} a_i 2^i + \sum_{i=0}^{n-1} b_i 2^i + c_0 = \sum_{i=0}^{n-1} (a_i + b_i) 2^i + c_0$$

Starting from the least significant position ($i = 0$) we can convert

$$a_0 + b_0 + c_0 = 2c_1 + s_0 \quad \text{or in general for } i = 0, \dots, n-1: \quad a_i + b_i + c_i = 2c_{i+1} + s_i$$

Substituting we have
$$s = \sum_{i=0}^{n-1} (a_i + b_i) 2^i + c_0 = c_n 2^n + \sum_{i=0}^{n-1} s_i 2^i$$

 - Ripple-carry implementation of an n-bit adder built from 1-bit adders:
- Time taken for the carry to propagate from c_0 to c_n is proportional to n : $t_n = n \cdot t_1$



7.4 2's complement representation of numbers

- The 2's complement number system is an extension of a binary system to representation of also the negative numbers
- In the 2's complement system the most significant weight is negative, or alternatively the most significant digit (the sign digit) takes values $a_{n-1} \in (-1, 0)$

- Hence, an n -bit numeral $\mathbf{a} = (a_{n-1}, a_{n-2} \dots a_0)$ represents the number:

$$a = -a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$$

All 3-bit 2's complement numbers:

- Example:

$$a = \underbrace{[\bar{1}0110]}_{A_{4:0}} \begin{bmatrix} 2^4 \\ 2^3 \\ 2^2 \\ 2^1 \\ 2^0 \end{bmatrix} = -2^4 + 2^2 + 2^1 = -(10)_{10}$$

-421	a
000	0
001	1
010	2
011	3
100	-4
101	-3
110	-2
111	-1

- The range of numbers represented is from $(10 \dots 0)_2 = -2^{n-1}$ to $(01 \dots 1)_2 = 2^{n-1} - 1$

7.5 Changing sign of a 2's complement number

- Complementing every digit of a 2's complement number: (Note that $\bar{a}_i = 1 - a_i$)

$$\bar{a} = -(1 - a_{n-1})2^{n-1} + \sum_{i=0}^{n-2} (1 - a_i)2^i = -2^{n-1} + \sum_{i=0}^{n-2} 2^i + a_{n-1}2^{n-1} - \sum_{i=0}^{n-2} a_i 2^i$$

Re-grouping the terms and noting that $\sum_{i=0}^{n-2} 2^i = 2^{n-1} - 1$, we have

$$\bar{a} = -1 - (-a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i) = -a - 1$$

or

$$-a = \bar{a} + 1$$

- Hence, to change the sign of a 2's complement number we **complement each digit and add 1:**

$$\begin{array}{r} \text{---}32168421\text{---} \\ a = 101100 = -32+12 = -20 \\ \bar{a} = 010011 \\ +1 \quad \quad \quad 1 \\ \hline -a = 010100 = +20 \end{array}$$

- **Sign extension:**

Note that increasing the number of bits we have extend to the left the bit sign.

For example: $(10011)_2 = (1111110011)_2$ and $(010011)_2 = (0000010011)_2$

7.6 Adding 2's complement numbers

- 2's complement n -bit numbers can be added using a standard binary adder. The n -bit result will be correct provided that the **overflow** does not occur.
- Formal proof:

$$s = a + b + c_0 = -a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i2^i - b_{n-1}2^{n-1} + \sum_{i=0}^{n-2} b_i2^i + c_0 = -(a_{n-1} + b_{n-1})2^{n-1} + \sum_{i=0}^{n-2} (a_i + b_i)2^i + c_0$$

Substituting the 1-bit addition law

$$a_i + b_i + c_i = 2c_{i+1} + s_i, \quad \text{we have}$$


$$s = -(a_{n-1} + b_{n-1})2^{n-1} + 2c_{n-1}2^{n-2} + \sum_{i=0}^{n-2} s_i2^i = c_{n-1}2^n - (a_{n-1} + b_{n-1} + c_{n-1})2^{n-1} + \sum_{i=0}^{n-2} s_i2^i$$

Finally, we have

$$s = a + b + c_0 = (c_{n-1} - c_n)2^n - s_{n-1}2^{n-1} + \sum_{i=0}^{n-2} s_i2^i$$

- When $c_{n-1} = c_n$ the above expression gives the proper 2's complement sum of a and b (and c_0)
- When $c_{n-1} \oplus c_n = 1$ **overflow** occurs and the result is "incorrect", that is, $\pm 2^n$ must be added for proper interpretation of the result

 Ripple-carry implementation of an n -bit 2's complement adder:



Examples:

$\begin{array}{r} -168421 \\ \hline 11011 = -5 \\ 01011 = 11 \\ \hline \textcircled{1}\textcircled{1}0110 \text{ CARRY} \\ \hline 00110 = +6 \\ \hline \text{NO OVERFLOW} \end{array}$	$\begin{array}{r} -168421 \\ \hline 00101 = +5 \\ 01101 = +13 \\ \hline \textcircled{0}\textcircled{1}1010 \text{ CARRY} \\ \hline 10010 = -14 \\ \hline \text{OVERFLOW} \end{array}$	$\begin{array}{r} -168421 \\ \hline 10110 = -10 \\ 10011 = -13 \\ \hline \textcircled{1}\textcircled{0}1100 \text{ CARRY} \\ \hline 01001 = +9 \\ \hline \text{OVERFLOW} \end{array}$
--	---	---

Note that:


- An overflow can only occur when we are adding numbers of **the same sign**.
- In this case the c_n carry is equal to the sign bit but the c_{n-1} carry can be both 0 or 1.
- Adding numbers of opposite sign the c_{n-1} carry propagates through the sign position and $c_n = c_{n-1}$

7.7 Carry propagation and generation

- Designing adders it is useful to formulate the following carry propagation/generation conditions.
- Consider again a 1-bit adder in which input and output variables are related by the following equation:

$$2d + s = a + b + c$$

- **Carry propagation:** when $a \oplus b = 1$ (a and b are **different**)
 $d = c$ output carry is equal to the input carry.
- We say that the carry $c = d$ **is propagated through** this position of the adder.
- **Carry generation:** when $a \oplus b = 0$ (a and b are **identical**)
 $d = a, s = c$ output carry is equal to the addend bit $a = b$ and is independent of the input carry c .
- We say that the carry $d = a$ **is generated** at this position of the adder.

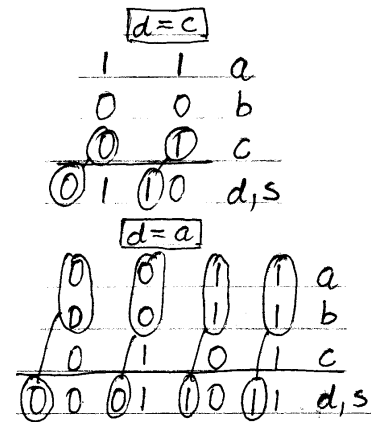

- Using two intermediate signals:
- the logic **equations for the 1-bit adder** can be written as:

$$g = a \cdot b \quad \text{— carry "1" generate}$$

$$p = a \oplus b \quad \text{— carry propagate}$$

$$s = p \oplus c \quad \text{— the sum}$$

$$d = g + p \cdot c \quad \text{— the output carry}$$

7.8 Carry Lookahead adder

- The ripple-carry n -bit adder is relatively slow, because the initial carry c_0 must travel through all n 1-bit adders.
- This can be avoided if we unfold the recursive way of calculating carry.
- This can be conveniently done using carry generate/propagate signals:


$$c_1 = g_0 + p_0 \cdot c_0$$

$$c_2 = g_1 + p_1 \cdot c_1 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0$$

$$c_3 = g_2 + p_2 \cdot c_2 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0$$

...

 - Note from the logic diagram that the number of gates to produce the carry signal for the given position and their number of inputs grows with the adder position number
- Such an adder implementation is called a carry look-ahead adder and is the typical way of speeding up the adder operations.




7.9 Subtractors

- Subtractors are typically used in the 2's complement system.
- Implementations of a subtractor involves the change of sign of the subtrahend through the complementation of its bits and an increment, according to the formula:

$$s = a - b = a + \bar{b} + 1$$

- the resulting block/logic diagrams:

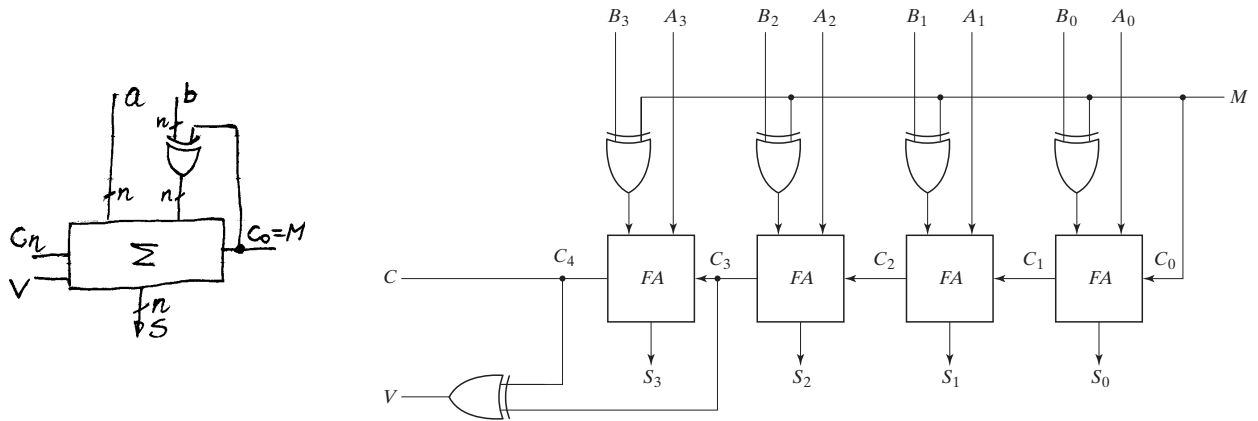


- It is also possible to build a (i-bit) subtractor according to the formula: $-2d + s = a - b - c$
- Note that the weight associated with carry is negative.

Give the truth table and logic equation for such a subtractor. Compare it with a 1-bit adder.

 7.10 VHDL specification of a 1-bit adder

The 1-bit adder entity specifies input output ports:



```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
ENTITY add_1b IS
    PORT (a, b, c : IN bit ;
          s, d : OUT bit ) ;
END add_1b ;
```



Many architectures are possible. Consider the following two:

```
-- dataflow architecture for add_1b
ARCHITECTURE d_flow_a OF add_1b IS
BEGIN
    s <= a XOR b XOR c ; -- a SIGNAL assignment
    d <= (a AND b) OR ((a OR b) AND c) ;
END d_flow_a ;

  -- another dataflow architecture for add_1b
ARCHITECTURE d_flow_b OF add_1b IS
    SIGNAL e : std_logic ; -- internal signal declaration
BEGIN
    e <= a XOR b ;
    s <= e XOR c ;
    d <= (a AND b) OR (e AND c) ;
END d_flow_b ;
```



- In the `d_flow_b` architecture we use an internal **signal** `e` which is specified as being of the type `std_logic`.
- The internal signals are always bi-directional and are used to simplify the description of the circuit.

Two more architectures:

In this architecture we specify the 1-bit adder in the form of its truth table. The truth table can be specified as a **constant array of binary words**:

```

ARCHITECTURE ttbl OF add1_b IS
  TYPE arr_vec IS ARRAY (natural range <>)
    OF std_logic_vector(1 downto 0);
  CONSTANT add1bit : arr_vec(0 to 7) := (
    -- d s      cba
    ----- the truth table of a 1-bit adder
    "00", -- 0 0
    "01", -- 1 1
    "01", -- 2 1
    "10", -- 3 2
    "01", -- 4 1
    "10", -- 5 2
    "10", -- 6 2
    "11"); -- 7 3
  SIGNAL cba : std_logic_vector (2 downto 0) ;
  SIGNAL ds : std_logic_vector (1 downto 0) ;
BEGIN
  -- concatenation of three signals into one 3-bit word
  cba <= c & b & a ;
  -- reading from the truth table
  ds <= add1bit(conv_integer(unsigned(cba)));
  d <= ds(1) ;
  s <= ds(0) ;
END ttbl ;
    
```

The 1-bit adder can be also specified arithmetically, leaving all the design/synthesis problems to the CAD tools:

```


ARCHITECTURE cnt1 OF add_1b IS
  SIGNAL ds : std_logic_vector (1 downto 0) ;
BEGIN
  ds <= unsigned('0' & a)
    + unsigned('0' & b)
    + unsigned('0' & c) ;
  d <= ds(1) ;
  s <= ds(0) ;
END cnt1 ;
    
```

- Note the various type conversion functions: `unsigned` and `conv_integer`.
- Type conversion informs the tools about desired method of conversion of binary vectors into numbers.

 7.11 Arithmetic-Logic Units

- In practical applications adders and subtractors are group together with logic functions performed on n -bit binary words.


- As an example we consider an ALU performing eight different arithmetic and logic operations selected by a 3-bit operation code, `opc(2:0)`



- The i -th bit of the ALU can have the following logic structure:

opc	function
0 0 0	$a + b + c_0$
0 0 1	$a \oplus b$
0 1 0	$a \text{ OR } b$
0 1 1	$a \cdot b$
1 0 0	$a - b - c_0$
1 0 1	$\overline{a \oplus b}$
1 1 0	$\overline{a \cdot b}$
1 1 1	$a \text{ OR } b$

 - The operations performed are described by the following table:



7.12 VHDL implementation of n -bit arithmetic circuits. The “generate” statement.


- In VHDL 1-bit arithmetic circuits are replicated to form a n -bit circuit using the **generate** statement of the form: **for ... generate**
- The **generate** statement is a loop which replicates the **circuitry** specified by its body.
- Consider again a 4-bit incrementer as an illustrative example
- The **generate** loop will be repeated 4 times, and its body will describe the 1-bit incrementer in the following way:

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all;
ENTITY incr4b IS
  GENERIC (N : natural := 3) ;
  PORT (
    a : IN  std_logic_vector (N downto 0) ;
    c0 : IN  std_logic ;
    y : OUT std_logic_vector (N downto 0) ;
    d : OUT std_logic ) ;
END incr4b ;

ARCHITECTURE GnrStt OF incr4b IS
  SIGNAL c : std_logic_vector (N+1 DOWNTO 0) ;
BEGIN
  c(0) <= c0 ;
  gnrt: FOR i IN 0 TO N GENERATE
    y(i) <= a(i) XOR c(i) ;
    c(i+1) <= a(i) AND c(i) ;
  END GENERATE gnrt ;
  d <= c(N+1) ;
END GnrStt ;

```

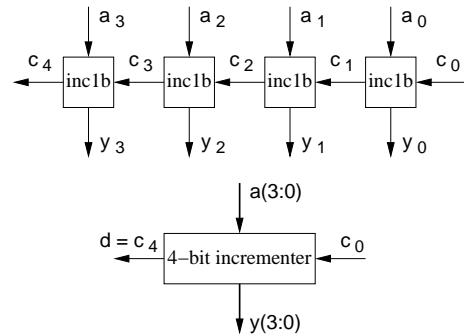

1-bit incrementer:

$$y_i = a_i \oplus c_i, \quad c_{i+1} = a_i \cdot c_i$$

- Note that the architecture consists of three **concurrent** statements (two assignment statements and one generate statements) that can be written in any order.
- Similarly, two assignment statements inside the generate statement can be also written in any order.

7.13 Structural specification of digital circuits

- In the previous examples VHDL statements described signal flow inside a component (logic circuit).
- It is possible to describe a digital circuit as interconnection of other components.
- Each constituent component is a black box with an unspecified, at this stage, function or behaviour, but with precisely defined ports.
- In the declarative part of the architecture we specify input-output ports of all components used in the architecture body in a way identical to the respective entity declarations for these components.
- The components may already exist in libraries, or can be specified later.
- Such structural specification of digital circuits is made in VHDL with the **Component Instantiation Statement** of the general form:

port map (...)

We use the n -bit incrementer to clarify the concept of structural specification.

We start with specification of a 1-bit incrementer as a separate component:

```
ENTITY inclb IS
  PORT ( a, c : IN std_logic ;
        d, y : OUT std_logic ) ;
END inclb ;

ARCHITECTURE arch1 OF inclb IS
BEGIN
  y <= a XOR c ;
  co <= a AND c ;
END arch1 ;
```

Note that

- In the architecture body the library components are instantiated as many times as specified by the schematic describing the architecture using a port map component instantiation statement.
- Each component instantiation statement is labeled as its schematic equivalent. In the example, the 1-bit component is labeled `u1`
- Interconnections between components are specified by the port map statement. For it to work, every net in the schematic, that is, all external and internal signals, must be assigned a name.
- Every port map statement is associated by positions with the respective component declaration.

A.P. Papliński

7–19

Note also

- In the **generate** statement we used expression “`a’range`” to describe the scope of the generate loop. It is an example of an **attribute** that we will study in some depth latter. Here we simply have:

$$\mathbf{a'range} \equiv \mathbf{3\ downto\ 0}$$

- In the **port map** statement every signal is associated with the respective formal component port by position, in this case according to the following table

component:	a	c	d	y
port map:	a(i)	c(i)	c(i+1)	y(i)

- There is another, more explicit form of the **port map** statement where association of the formal component ports and the instantiated component signals is by names, not by position.

We can write

```
PORT MAP ( a => a(i), c => c(i), d => c(i+1), y => y(i));
```