 


## 8 Design Example: A Division-by-Constant Combinational Circuit

### 8.1 A general case

A combinational circuit which divides n-bit binary number by a ‘small’ constant  $\beta$  has a modular structure of an iterative 1-D array circuit, similar to the structure of an incrementer or an adder. The carry propagates from left to right, and its values are limited by the divisor,  $\beta$ .



Input/output variables are related by the following equation which links divider, divisor, quotient and remainder:

$$\frac{2^n \cdot c_n + a}{\beta} = s + \frac{c_0}{\beta}$$

or


$$2^n \cdot c_n + a = \beta \cdot s + c_0$$

- The objective is to build a combinational circuit, which, given n-bit input  $a$  and possibly  $c_n$ , will generate the quotient  $s$  and the remainder,  $c_0$ .
- It is possible to build such a circuit using 1-bit cells.
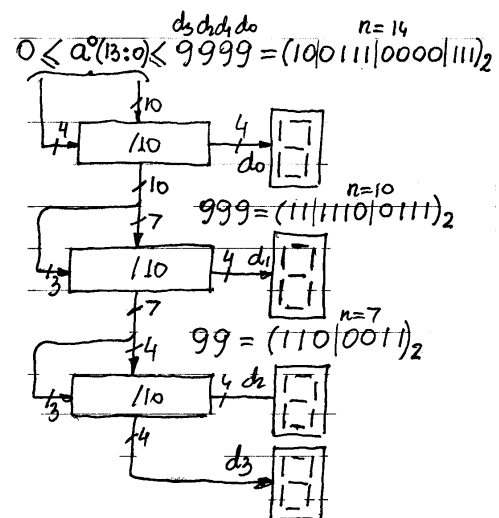
### 8.2 Binary-to-decimal conversion

- The division-by-constant circuit can be used for binary-to-decimal conversion.
- It is the “division-by-target” radix method, therefore  $\beta = 10$ .

- In the example we consider conversion of a binary number to a 4-digit decimal number.
- The largest 4-digit decimal number, 9999, is represented by a 14-bit binary number.
- The first level division-by-10 circuit generate the first digit  $d_0$  as a remainder and a 10-digit quotient that is equivalent to 3-digit decimal number not greater than 999.
- The final level division-by-10 circuit generate two last decimal digits,  $d_3, d_2$




### 8.3 A 1-bit division-by-constant circuit

- Consider as an example a division-by-3 circuit. In this case, we have

$$n = 1; \quad \beta = 3; \quad m = 2; \quad \{2^m \geq \beta\}$$

 - Input and output carry signals,  $c, d$ , are 2-bit numbers which are less than the divisor,  $\beta = 3$ , that is:
- The I/O equation is now of the following form:



$$c, d \in \{0, 1, 2\}$$

$$2 \cdot c + a = 3 \cdot s + d$$

Function Table

| $c$ | $a$ | $2c + a$ | $3s + d$ | $s$ | $d$ |
|-----|-----|----------|----------|-----|-----|
| 0   | 0   | 0        | 0        | 0   | 0   |
| 0   | 1   | 1        | 0        | 0   | 1   |
| 1   | 0   | 2        | 0        | 0   | 2   |
| 1   | 1   | 3        | 1        | 0   | 0   |
| 2   | 0   | 4        | 1        | 1   | 1   |
| 2   | 1   | 5        | 1        | 2   | 0   |
| 3   | 0   | 6        | —        | —   | —   |
| 3   | 1   | 7        | —        | —   | —   |

Truth Table

| $c_1$ | $c_0$ | $a$ | $s$ | $d_1$ | $d_0$ |
|-------|-------|-----|-----|-------|-------|
| 0     | 0     | 0   | 0   | 0     | 0     |
| 0     | 0     | 1   | 0   | 0     | 1     |
| 0     | 1     | 0   | 0   | 1     | 0     |
| 0     | 1     | 1   | 1   | 0     | 0     |
| 1     | 0     | 0   | 1   | 0     | 1     |
| 1     | 0     | 1   | 1   | 1     | 0     |
| 1     | 1     | 0   | —   | —     | —     |
| 1     | 1     | 1   | —   | —     | —     |


- From the tables the logic equations for the three outputs can be derived using the Karnaugh map technique.
- One possible SoP form is as follows:

$$s = c_1 + a \cdot c_0$$

$$d_1 = \bar{a} \cdot c_0 + a \cdot c_1$$

$$d_0 = \bar{a} \cdot c_1 + a \cdot \bar{c}_1 \cdot \bar{c}_0$$

 A possible VHDL implementations of the 1-bit cell, **div3b1** based on the derived logic equations is as follows:



```

LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

-- div3b1, 1-bit div-by-3 Entity Description
ENTITY div3b1 IS
    PORT (
        c : IN  std_logic_vector (1 downto 0) ;
        a : IN  std_logic ;
        d : OUT std_logic_vector (1 downto 0) ;
        s : OUT std_logic
    );
END div3b1;

-- arch1 Architecture Description
ARCHITECTURE arch1 OF div3b1 IS

    BEGIN
        s <= c(1) or (a and c(0)) ;
        d(1) <= (not a and c(0)) or (a and c(1)) ;
        d(0) <= (not a and c(1)) or (a and not c(1) and not c(0)) ;
    END arch1 ;

```

- At this stage we might like to avoid deriving the logic equations and use the truth table directly, as in the 1-bit adder example.
- We specify the **truth table as a constant** as it is illustrated in the next section.

#### 8.4 An architecture with the truth table specification

- The truth table is simply specified as a constant **array of binary words**. The array consists of  $2^3$  3-bit words as in the truth table on page 8–3.

```

ARCHITECTURE dv3tt OF div3b1 IS
  TYPE arr_vec IS ARRAY (natural range <>)
    OF std_logic_vector(2 downto 0);
  CONSTANT sd_ac : arr_vec := (
    -- sd1d0      ca
    ----- the truth table:
    "000", -- 0
    "001", -- 1
    "010", -- 2
    "100", -- 3
    "101", -- 4
    "110", -- 5
    "----", -- 6
    "----"); -- 7
  SIGNAL sd : std_logic_vector (2 downto 0) ;
BEGIN
  -- reading from the truth table :
  sd <= sd_ac(conv_integer(unsigned(c & a)));
  d <= sd (1 downto 0) ;
  s <= sd (2) ;
END dv3tt ;

```

- The truth table is a constant **sd\_ac** of the type **arr\_vec**.
- The value of the constant is our truth table. Note that we can also specify the “don’t care” values, ‘-’.
- To read the values from the truth table we need an assignment statement of the form
 

```
sd <= sd_ac(ca);
```
- In the **array** specification we have implicitly specified that the address signal **ac** is of the **type integer**.
- Therefore, we first concatenate (**c & a**) into a 3-bit **std\_logic\_vector**, which is subsequently converted into a 3-bit **unsigned** vector that can be converted into an integer.

- The conversion functions are specified in the libraries **ieee.std\_logic\_1164** and **ieee.std\_logic\_arith**.

- We consider another architecture of the 1-bit division-by-3 circuit, based on the division and remainder operations.

Such operators are available in the **numeric\_std** IEEE library.

- The division ‘/’ and remainder **rem**, like all other arithmetic operators, do not operate on signals of the type **std\_logic\_vector**. Instead, we can use signals of the type **unsigned**.
- The conversion function **std\_logic\_vector** converts signals back from the **unsigned** to **std\_logic\_vector** form.
- Since **ca** is a 3-bit signal, the results of division and remainder operations are also 3-bit signals.

```


LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

-- div3b1, 1-bit div-by-3 Entity Description
ENTITY div3b1b IS
  PORT(
    c : IN  std_logic_vector (1 downto 0) ;
    a : IN  std_logic ;
    d : OUT std_logic_vector (1 downto 0) ;
    s : OUT std_logic
  );
END div3b1b;
ARCHITECTURE dv3mod OF div3b1b IS
  SIGNAL ca : unsigned (2 downto 0);
  SIGNAL ss, dd : std_logic_vector (2 downto 0);
BEGIN
  ca <= unsigned(c & a) ;
  dd <= std_logic_vector(ca REM 3) ;
  d <= dd(1 downto 0) ;
  ss <= std_logic_vector(ca/3) ;
  s <= ss(0) ;
END dv3mod ;

```
 
### 8.5 An n-bit division-by-three circuit

- In order to implement an n-bit division-by-3 circuit, we can instantiate the 1-bit component `div3b1` using the **port map** and **generate** statements.
- The resulting structure of a 4-bit division-by-3 circuit has the following block-diagram:



- The numbers represented by the port signals are related by the following arithmetic equality:

$$16 \cdot ec + ea = 3 \cdot es + ed$$

- The internal carry signals, `cc`, form a 5 by 2 array of 2-bit signals.

The block diagram of the 4-bit division-by-3 circuit is equivalent to the following VHDL code:

A.P. Papliński

8-7

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
ENTITY div3b4 IS --- 4-bit division-by-3
  GENERIC (N : natural := 3, m : natural := 1) ;
  PORT (
    ec : IN std_logic_vector(m downto 0) ;
    ea : IN std_logic_vector(N downto 0) ;
    ed : OUT std_logic_vector(m downto 0) ;
    es : OUT std_logic_vector(N downto 0) );
END div3b4;
ARCHITECTURE strctrl OF div3b4 IS
  COMPONENT div3b1
    PORT (
      c : IN std_logic_vector(1 downto 0) ;
      a : IN std_logic ;
      d : OUT std_logic_vector(1 downto 0) ;
      s : OUT std_logic
    ) ;
  END COMPONENT div3b1 ;
  TYPE arr5b2 IS ARRAY(4 downto 0)
    OF std_logic_vector(1 downto 0);
  SIGNAL cc : arr5b2 ;
BEGIN
  cc(4) <= ec ;
  glp: FOR i IN ea'RANGE GENERATE
    U1: div3b1
      PORT MAP ( c => cc(i+1),
                a => ea(i),
                d => cc(i),
                s => es(i)
              );
  END GENERATE ;
  ed <= cc(0) ;
END strctrl ;

```

#### Note that

- In the **generate** statement `ea'range` is equivalent to `4 downto 0`.
- In the component instantiation statement, **port map**, we have used the association-by-name method.

A.P. Papliński

8-8