


## 9 Sequential Circuits

- In **combinational circuits** the output signals depend on current values of input signals.
- Past values of input signals do not have any influence on the current values of the output signals.
- In this sense, processing of input signals in combinational circuit is performed in a single time step.
- Combinational circuits are **static systems**.
- In **sequential circuits** input signals are processed in a multi-step way, so that output signals depend not only on **current**, but also on the **past** values of the **input signals**.
- This time dependency is implemented using the concept of internal **state signals**.
- Sequential circuits are dynamic systems, and their formal description is given by a model of a finite state machine.
- Any sequential circuit can be ultimately reduced to a single finite state machine. Therefore, these two terms are formally synonymous.
- Sequential circuits are hierarchically classified into the following groups with respect to their growing structural complexity:
  - Latches and flip-flops,
  - Registers and counters,
  - Algorithmic State Machines,
  - Processors, consisting of a datapath and a control unit.
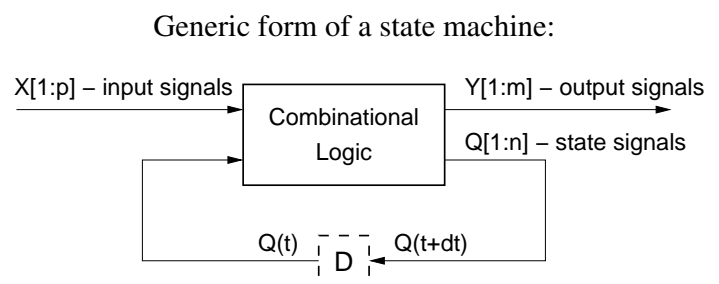
### 9.1 Finite State Machines

A finite state machine can be always reduced to

- a combinational logic block,
- feedback paths, possibly with delay elements in them



Note  $p$  **input signals**,  $X$ ,  $n$  **state signals**,  $Q$ , and  $m$  **output signals**,  $Y$ .

The combinational block has  $p + n$  inputs and  $m + n$  outputs.

- The input, state and output signals are related by the following well known equations:

$$Q(t + dt) = f(Q(t), X(t)) \quad \text{state equation} \quad (9.1)$$

$$Y(t) = g(Q(t), X(t)) \quad \text{output equation} \quad (9.2)$$

- The **state equation** says that the “next” values of the state signals  $Q(t + dt)$  are a function  $f$  of the current values of state signals  $Q(t)$  and input signals  $X(t)$ .
- The value of  $dt$  describes the delay in the feedback loop and can be controlled by an additional delay element  $D$ .
- Every **combination of state signals** is called the **state** of the state machine.

With  $n$  state signal the maximum number of **different states** is  $2^n$ .

- The **output equation** says that the current values of output signals  $Y(t)$  are a function  $g$  of the current values of state signals  $Q(t)$  and input signals  $X(t)$ .
- Note that the state transition function,  $f$ , and the output function,  $g$ , are **combinational** functions and “sequencing” is the result of the **feedback** loops.
- Functions  $f$  and  $g$  are often described in a tabular form. Such tables are called the **state transition table**, and **output table**, respectively.
- If the output function in eqn. (9.2) is of the form

$$Y(t) = g(Q(t)) \quad (9.3)$$

then the state machine is called a **Moore state machine**.

- In simple cases, the output signals,  $Y$ , can be just a subset of the state signals,  $Q$ .
- Note that in a Moore state machine output signals are independent of input signals.
- In a general case as in eqn. (9.2), when output signals depend both on input and state signals, the machine is called a **Mealy state machine**.
- It can be shown that from the purely formal point of view both versions are equivalent and can be converted to each other.
- From the point of view of the way the states evolve with time, the state machines are classified into two groups named asynchronous and synchronous.

### 9.1.1 Asynchronous state machines/sequential circuits

can be characterized by the following properties

- there are no delay elements in the state signals feedback loops, and, as a result, the delay  $dt$  in eqn (9.1) is “irregular” and depends on the internal delays of the components forming the combinational block,
- after a change of a state or input signal, the change of the states (state signals) occurs instantaneously, after the internal delay  $dt$  of the combinational block,
- because of this property, it is difficult to design a stable asynchronous state machine.
- Typically, asynchronous state machines used to build simple sequential circuits like **latches** and **flip-flops**.

A **necessary** condition for an asynchronous state machine to be **stable**, is that there must exist combinations of input and state signals such that the **next state**  $Q(t + dt)$  is identical with the **current state**  $Q(t)$ .

A **necessary** condition for an asynchronous state machine to **move correctly between states** is that during any transition **only one** state signal may be changed.

Otherwise we have a race between state signals and the final state will be unpredictable.

- For brevity, the current state  $Q(t)$  and the next state  $Q(t + dt)$  are often denoted  $Q$  and  $Q^+$ .

### 9.1.2 Synchronous (clocked) state machines

- are characterized by a fixed delay in the feedback path and, as a result, the change of states occurs only on the rising (falling) edge of the **clock signal**.


In other words, the clock frequency,  $f_c$ , specifies the delay  $dt = 1/f_c = t_c$

The state equation is written in the following form  $Q(t + 1) = f(Q(t), X(t))$  (9.4)

where  $t$  is now an integer numbering the clock period instances.

- We will see that the delay block in the general state machine is replaced with a **state registers Q** triggered by a specialised input signal, the **clock signal**,  $clk$ .
- A combinational circuit converts  $p$  **input signals** and  $n$  **state signals** into  $m$  **next state signals**.
- The register  $Q$  holds the state signals steady between the clock edges, that is for one clock cycle.
- A register in itself is a simple sequential circuit.

A generic synchronous sequential block:

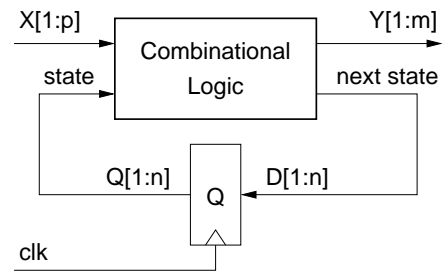

## 9.2 Latches

Latches are the simplest **bi-stable** (two states) asynchronous sequential circuits and are structurally characterized by the presence of a **single feedback loop** for the single state signal,  $Q$ .


The output signal is identical with the state signal, hence latches are Moore state machines.
 
### 9.2.1 S-R Latch

The S-R latch has **two inputs**:  $S$  – set and  $R$  – reset, and one **state signal**  $Q$  which is also the output signal.



Operations of the latch are best described by its **state (transition) diagram** which shows how the states evolves for differen values of the input signals.




The state diagram clearly shows that there are two stable states,  $Q = 0$  and  $Q = 1$ .

- The state diagram can now be converted into the **state table**.
- The table shows what is the **next state**  $Q^+$  for the **current state**  $Q$  and all combinations of **input signals**.
- Note that the signal  $S = 1$  moves the latch to the  $Q = 1$  state, whereas the signal  $R = 1$  moves the latch to the  $Q = 0$  state.
- Situation when both input signals are high,  $S \cdot R = 1$ , results in don't care conditions.



$S$	$R$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	*
1	1	1	*

 - From the **state table** we can obtain the **state equations**  $Q^+ = f(Q, S, R)$  using any minimization method, e.g. a Karnaugh map and subsequently the logic structure of the latch,
- Note the cross-coupled pair of NOR gates.




$$Q^+ = \overline{R} \cdot (S + Q)$$

$$= R + (S + Q)$$

  

 Finally, the S-R latch can be described through the time waveforms:




**Exercise:**


For a dual cross-coupled pair of NAND gates derive the state equations, state table and state diagram.

 9.2.2 D Latch

- The D latch has **two inputs**:  $D$  – data and  $Ld$  – load, and one **state signal**  $Q$  which is also the output signal.



 - The operations if the **D latch** can be best described by the **state diagram**:  
 When  $Ld = 0$ , the latch maintains its current states.  
 When  $Ld = 1$ , the latch moves to the state:  $Q \leq D$ , that is, it stores data  $D$  in its internal state  $Q$ .




- From the state diagram we can obtain by the following **state tables**, which give the values of the **next state signal**,  $Q^+$ , as a function of the **current state signal**,  $Q$ , and input signals  $Ld, Q$ :
- As previously, the state table can be converted in the state equations and subsequently into the logic structure of the latch

$Ld$	$D$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


A possible implementation:

$Q^+$	$D$			
	0	0	1	0
$Q$	1	1	1	0
	$Ld$			
 
$$Q^+ = \overline{Ld} \cdot Q + Ld \cdot D$$




Waveforms:

 
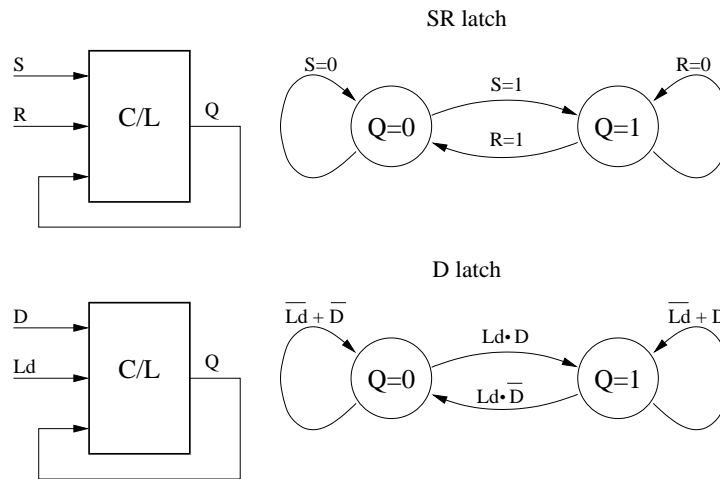
### 9.2.3 Latches — Summary


State Transition Diagrams for the SR and D latches:



C/L stands for “combinational logic”

- Note that a latch stores 1-bit data.

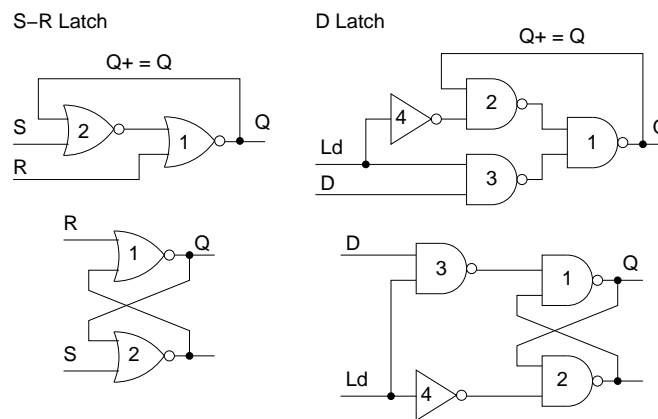Possible logic diagrams of the S-R and D latches:



The latches are referred to as the **level-sensitive** devices:

when the Ld signal is high, every change of the input D is immediately stored in (transfer to) the latch output, Q.

## 9.2.4 VHDL description

- In order to write a VHDL specification of a latch we can use its state table or any equivalent logic equation.
- For example, a possible description of the S-R latch using it's “next-state” equation can have the following form:

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;


ENTITY LchSR IS
  PORT (S, R : IN std_logic ;
        Q : OUT std_logic );
END Lchsr ;

ARCHITECTURE nors OF Lchsr1 IS
  SIGNAL Qi : std_logic ;
BEGIN
  Qi <= not ( R or not( S or Qi) ) ;
  Q <= Qi ;
END nors ;
```

- Note that since the port signal  $Q$  is an output signal it **cannot** be used in expressions.
- Therefore, we have to introduce an internal signal  $Qi$  identical in behaviour to  $Q$ .


## 9.2.5 Simulation waveforms

- Simulation waveforms for an S-R latch

 


- As expected signal  $R$  resets the state of the latch ( $Q=0$ ) and  $S$  sets the state to ( $Q=1$ ).
- When both  $R$  and  $S$  are HIGH, the latch goes to ( $Q=0$ ).

- Simulation waveforms for the D latch:

 
 
### 9.3 Flip-Flops


- **Latches**, being level-sensitive devices, cannot be easily used to form more complex sequential circuits.
- Consider, for example a circuit in which the complement of the output of the D latch is fed back as the input signal.
- The resulting behaviour is oscillatory for  $Ld = 1$ , because of the loop that goes through three inverting gates.



- **Flip-Flops are edge-sensitive** devices.
- The change of the flip-flop state can occur only as the result of the (positive/rising) **edge of the clock signal** that synchronizes the work of the flip-flop.

 
### 9.4 D Flip-Flop

- The D Flip-Flop (D FF) is the most fundamental sequential circuit.
- It is the building block of registers, counters and synchronous state machines.
- The symbol, operation/function table and the behaviour of the D Flip-Flop:



clk	operation
↑	$Q \leftarrow D$
others	$Q \leftarrow Q$


- The D flip-flop is similar to the D latch in that that the input signal,  $D$ , is loaded into the FF ( $Q \leftarrow D$ ) under the control of the triggering signal ( $Ld$ , or  $clk$ ).
- Unlike in the latch, the load operation in flip-flops takes place only during the **rising edge** of the clock signal.
- Outside the triggering edge of the clock signal the flip-flop is insensitive to any changes at its D input as indicated in the timing diagram
- The waveforms illustrate the fact that the value of the input signal  $D$  at the rising edge of the clock, say,  $s1$ , is loaded into the flip-flop in that sense that  $Q = s1$ .
- Changes in  $D$  between the rising edges does not influence the state of the flip-flop.

 



- The state (transition) diagrams for synchronous circuits assume that any change of the state occurs only for the rising edge of the clock signal.
- Therefore, the clock signal is not shown in the state diagrams.

 - Hence, the state diagram for the D Flip-Flop as a synchronous state machine is very simple:



- Note some variation regarding description of the next-state conditions.  
We write for example  $D = 0$  or just  $\bar{D}$  whichever is more appealing to you.

#### 9.4.1 VHDL description of a D flip-flop

- The VHDL description of flip-flops is relatively simple but a few new language structures need to be used.
- Consider the following template describing the **D flip-flop**:
 

```


SIGNAL clk, D, Q : bit ;
...
PROCESS (clk)
BEGIN
  IF (clk'EVENT AND clk = '1') THEN
    Q <= D ;
  END IF ;
END PROCESS ;

```
- The **process** statement encapsulates **sequential statements**.
- The sensitivity list specify signals that are monitored for any change or modification
- In VHDL the edge-detection mechanism is provided by the **event** attribute.
- This attribute operates on a signal and returns a boolean value which is always **false**, unless the signal showed a change in value, that is a signal edge.
- $(\text{clk}'\text{EVENT AND clk} = '1')$  makes sure that it is the rising edge which is detected.
- Note also that only  $\text{clk}$  signal is on the process sensitivity list.
- The **if ... then** statement is a sequential statement.
- The **process** statement with the **if** statement makes sure that the assignment  $Q \leq D$  takes place after the rising edge of the clock is detected.
 
### 9.4.2 Logic synthesis of a D flip-flop

- The positive-edge-triggered **D flip-flop** (D-FF) is the simplest, but the most important **synchronous sequential circuit**, the building block of registers, counters and synchronous state machines.
- Internally, however, such a flip-flop is an asynchronous sequential circuit (state machine).
- The design procedure is similar to that outlined for the D latch.
- The first parameter to establish is the **number of states**, or state signals needed to describe the sensitivity to the clock edge.
- Although formal methods to find out the required number of states do exist, we will just try first if two state signals, that is, four states are sufficient.
- Solutions with three state signals also exist.

A block-diagram, the **state diagram** and the symbol of a **positive-edge-triggered D flip-flop**:




- There are **four states** coded by **two state signals**, **P** and **Q**.
- Two state signals are fed back to the inputs of the combinational circuit.
- There are two input signals, **D** (data) and **clk** (clock). The **Q** state signal is used as an output signal. Note that the state transition diagram satisfies the two necessary conditions for a “sensible” asynchronous state machine, namely, that
  - there are combinations of input and state signals such that the next state is identical with the current state, and that
  - during transitions between states only one state signal is being changed.


- The expected behaviour described by the state diagram is that during the **rising edge** of the clock signal the 1-bit data from the input  $D$  is loaded into the flip-flop, that is,

$$Q \leq D$$


- Outside the rising edge of the clock signal the state  $Q$  is to be unchanged, regardless of the variations of the  $D$  input and possibly the second state signal,  $P$ .
- Assume that we are in the state  $PQ = 00$ .  
If  $clk = 0$ , we remain in this state.  
If  $clk = 1$ , we go either to state  $PQ = 01$ , or  $PQ = 10$  depending on the value of the signal  $D$ .
- If  $clk = 1$  and we have just move to the state  $PQ = 01$  or  $10$ , we stay in such a state regardless of the value of the signal  $D$ .  
This describes the **positive-edge-triggered behaviour**.
- In states  $PQ = 01$  or  $10$  we wait for clock signal to go to zero and then we go either to the state  $PQ = 11$  or  $00$ , respectively.

 

Timing diagram:

 

 - The next step is to design a combinatorial circuit which implements the required behaviour of the flip-flop.
- For this, we convert the **state diagram** into the **state transition table**.



clk	D	P	Q	P+	Q+
0	-	0	0	0	0
1	0	0	0	1	0
1	1	0	0	0	1
0	-	0	1	1	1
1	-	0	1	0	1
0	-	1	0	0	0
1	-	1	0	1	0
0	-	1	1	1	1
1	0	1	1	1	0
1	1	1	1	0	1

- The state transition table describes the relationship between the current state signal,  $P, Q$ , the input signals,  $clk, D$ , and the next state signals  $P+, Q+$ .  
The symbol ‘-’ denotes the don’t care conditions.

- The state transition table is equivalent to the truth table for the following combinatorial circuits:

$$P+ = f_P(\text{clk}, D, P, Q)$$

$$Q+ = f_Q(\text{clk}, D, P, Q)$$

- If we aim at “manual” design, then the functions  $f_P$  and  $f_Q$  can be obtained from the following Karnaugh maps generated from the state transition table.

		P+			
clk D	PQ	00	01	11	10
00	00	0	0	0	1
01	01	1	1	0	0
11	11	1	1	0	1
10	10	0	0	1	1

		Q+			
clk D	PQ	00	01	11	10
00	00	0	0	1	0
01	01	1	1	1	1
11	11	0	0	0	0
10	10	0	0	1	1

- From the Karnaugh maps it is possible to derive a suitable gate implementation of the combinatorial part of the flip-flop.
- Two feedback loops, for  $P = P+$  and  $Q = Q+$ , complete the design.

If we decide that it would be more efficient to rely on the VHDL compiler to synthesize a good combinational circuit, then a relevant VHDL code could be of the following form:


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

-- D flip-flop described by the truth table
ENTITY Dfft IS
  PORT( clk, D : IN std_logic ;
        Q : OUT std_logic );
END Dfft;

ARCHITECTURE ttbl OF Dfft IS
  TYPE arr2d IS ARRAY (natural range <>,
                      natural range <>) OF std_logic;
  CONSTANT ttDff : arr2d(1 to 2, 0 to 15) := (
    -- truth table for P+ Q+
    --0123456789abcdef (P, Q, clk, D)
    "0010110000111110" , --1 P
    "0001111100001101" ); --2 Q
  SIGNAL P, QQ : std_logic ;
  SIGNAL S : std_logic_vector (3 downto 0) ;
  SIGNAL Si : integer range 0 to 15 ;
BEGIN
  S <= (P, QQ, clk, D) ;
  Si <= conv_integer(unsigned(S)) ;
  -- reading from the truth table
  P <= ttDff (1, Si) ;
  QQ <= ttDff (2, Si) ;
  Q <= QQ ;
END ttbl ;
```
 
### 9.4.3 Yet another implementation of a D flip-flop

- Another efficient implementation of a D flip-flop contains three state signals,  $S$ ,  $R$ ,  $Q$  as shown in the logic diagram.
- Three feedback loops are arranged so that the flip-flop consists of three interconnected S-R latches.
- Two “input” latches generates signals  $S$  and  $R$ , respectively, from the  $CLK$  and  $D$  input signals.
- The third, “output”, **low-level active** latch is driven by signals  $S$  and  $R$ .




#### Exercise

Consider an asynchronous sequential circuit with two inputs  $CLK$  and  $D$ , and two state signals  $S$  and  $R$  as in the logic diagram above.


- Derive the state diagram and the state table.  
Note that with two state signals there are four possible states.
 
### 9.5 The T flip-flop

- The T (**toggle**) flip-flop is the second most important one after the D flip-flop.
- The D flip-flop is the building block of the **registers**.
- The T flip-flop is the building block of the **counters**.
- The symbol, operation table and the state diagram of a **rising edge triggered T flip flop** are as shown:
- Remember that all state transitions/operations are performed at the rising edge of the clock signal.
- The principle of operation is simple: when the toggle signal is asserted ( $T = 1$ ) the rising edge of the clock signal changes the state of the flip-flop (the value of the state signal  $Q$ ) to the opposite value.
- Outside the rising edge, or when ( $T = 0$ ) the state remains unchanged.




$T$	operation
0	$Q \leq Q$ hold
1	$Q \leq \overline{Q}$ toggle

 
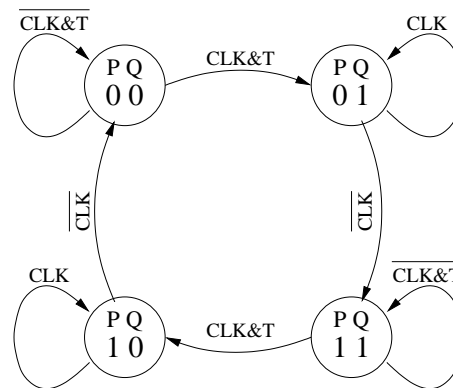
### 9.5.1 Logic synthesis of the T flip-flop

- In order to design the logic structure of the T flip-flop we start with its state diagram:
- Comparing with the D flip-flop the state diagram of the T flip-flop is slightly simpler which should result in a simpler implementation.
- In order to design the flip-flop we convert the state diagram into the state transition table, possible in the form of a Karnaugh map.



- The resulting map is as follows:
- From the above table we can derive the following logic equations:

$$P^+ = Q \cdot \overline{Clk} + P \cdot Clk$$

$$Q^+ = Q \cdot \overline{Clk} + Clk \cdot (T \cdot \overline{P} + \overline{T} \cdot Q)$$

		P <sup>+</sup> Q <sup>+</sup>			
Clk	T	00	01	11	10
PQ					
00	00	00	00	01	00
01	11	11	11	01	01
11	11	11	11	10	11
10	00	00	00	10	10

- The signal  $P^+$  can be generated using a 2-to-1 multiplexer driven by  $Clk$  which switches between  $Q$  and  $P$ .

### 9.5.2 Implementing the T flip-flop with a D flip-flop

- A T flip-flop can be built as a sequential circuit using a D flip-flop and a logic excitation circuit, as in the block-diagram.
- The **excitation table** is obtained from the **state table** and describes the value of the D flip-flop **input signal**  $D$  as a function of the **state signal**  $Q$  and the **input signal**  $T$ .

$$D = f(Q, T)$$

State table

T	Q	Q <sup>+</sup>
0	0	0
0	1	1
1	0	1
1	1	0

State equation:



$$Q^+ = T \oplus Q$$

Excitation table

T	Q	D
0	0	0
0	1	1
1	0	1
1	1	0

Excitation equation:


$$D = T \oplus Q$$

 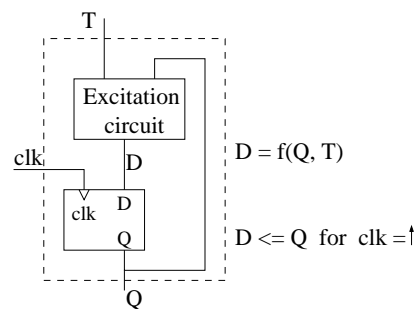
 
### 9.5.3 The T flip-flop as a frequency divider

One of the application of the T flip-flop is as a frequency divider.

Consider the following waveforms for  $T = 1$ :



Note that if the clock frequency is  $f_c$  and the frequency of the output signal is  $f_Q$ , then we clearly have

$$f_Q = \frac{1}{2}f_c$$


### 9.6 The JK flip-flop

- The JK flip-flop was popular some time ago and combines the functions of a SR and T flip-flops.
- In addition to the clock signal it has two inputs  $J$  (set) and  $K$  (reset) and its operations can be described by the following table:

C	J	K	OPERATION
not ↑	--	--	$Q \leftarrow Q$
↑	0	0	$Q \leftarrow Q$
↑	0	1	$Q \leftarrow 0$
↑	1	0	$Q \leftarrow 1$
↑	1	1	$Q \leftarrow \bar{Q}$

} HOLD  
RESET  
SET  
TOGGLE

 - Equivalently, the JK flip-flop can be described by the following (synchronous) state diagram in which transitions take place during the rising edge of the clock signal:




- The state diagram can be converted into the following (synchronous) state table:

J	K	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

HOLD  
RESET  
SET  
TOGGLE

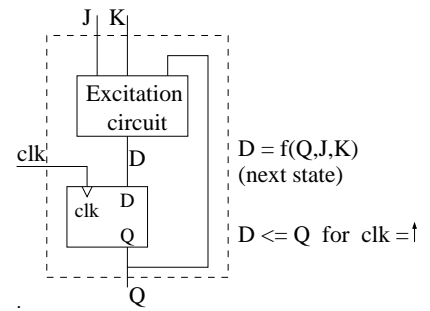- All synchronous (aka clocked) sequential circuits can be build using flip-flop(s), D flip-flop in particular, and a suitable excitation circuit which calculates the next state from the current state and input signals:




- If a D flip-flop is used, then the excitation table is identical to the state table,  $D$  replacing  $Q^+$ :
- The resulting excitation equation is as follows:

$$D = J \cdot \bar{Q} + \bar{K} \cdot Q = (J + Q) \cdot (\bar{K} \cdot \bar{Q}) = \overline{\overline{(J + Q)} + K \cdot Q}$$

J	K	Q	D	
0	0	0	0	HOLD
0	0	1	1	
0	1	0	0	RESET
0	1	1	0	
1	0	0	1	SET
1	0	1	1	
1	1	0	1	TOGGLE
1	1	1	0	

- A possible logic diagram follows:

 

### 9.7 Hazards in combinational and sequential circuits

as presented in sec. 9-7 of the textbook.