
 




## 10 Registers and counters
 
### 10.1 Registers


- The simplest  $n$ -bit register is a collection of  $n$  D flip-flops triggered by a common clock.
- I would prefer to call it just an  $n$ -bit D flip-flop, since it performs only a **load** operation on each rising edge of the clock.
- The simplest  $n$ -bit register should perform at least two operations **load** and **hold**
- This can be implemented in two ways:
  - blocking/gating the clock (typically a bad idea for a number of reasons)
  - adding an input multiplexer.



gated clock:

  

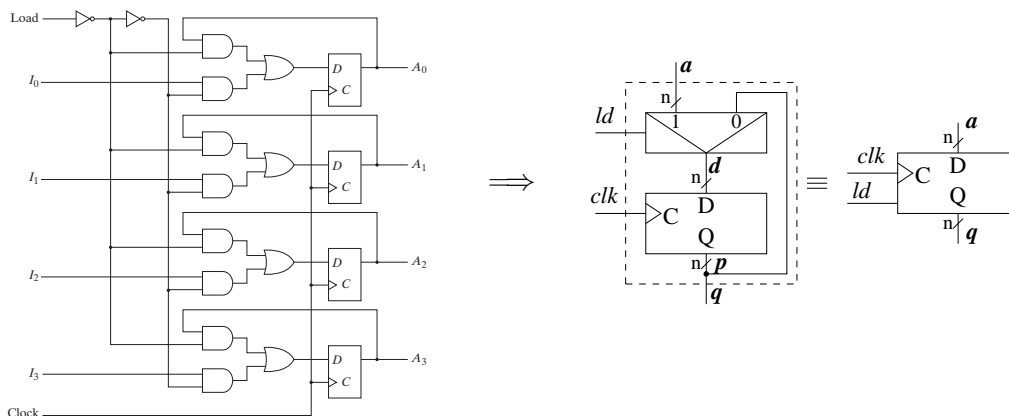
#### 10.1.1 An $n$ -bit “parallel load” register



The operation table of the  $n$ -bit register with parallel load:

load	operation	
0	$q \leftarrow q$	hold
1	$q \leftarrow a$	load

The timing diagram:

 

The VHDL architecture consists of three concurrent statements describing the input multiplexer, the flip-flop process and assignment of internal outputs from the flip-flops to the output port:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY plReg IS
  GENERIC ( N : integer :=4 );
  PORT ( clk, ld : IN std_logic ;
        A : IN std_logic_vector(N-1 downto 0) ;
        Q : OUT std_logic_vector(N-1 downto 0) );
END ENTITY plReg;

ARCHITECTURE rtl OF plReg IS
  SIGNAL P, D : std_logic_vector(A'RANGE) ;

BEGIN
  -- the input multiplexer:
  D <= A WHEN ld = '1' ELSE P ;

  -- internal signal on output port
  Q <= P ;

  -- the flip-flop process
  PROCESS (clk)
  BEGIN
    IF clk'EVENT AND clk='1' THEN
      P <= D ;
    END IF ;
  END PROCESS ;
END rtl ;


```

### 10.1.2 A simple shift register

- In general, a shift register allows the binary words stored in the register to be shifted left or right by one position, with additional bit being shifted in.
- The simplest shift register performs only one operation, say **shift-right**, at each rising edge of the clock, that can be described as (4-bit register has been assumed):


$$\begin{aligned}
 \mathbf{q} &\leq \text{shr}(\mathbf{sn}, \mathbf{q}), \quad \text{or} \\
 (q_3, q_2, q_1, q_0) &\leq (sn, q_3, q_2, q_1), \quad \text{or} \\
 q[3:0] &\leq (sn, q[3:1])
 \end{aligned}$$

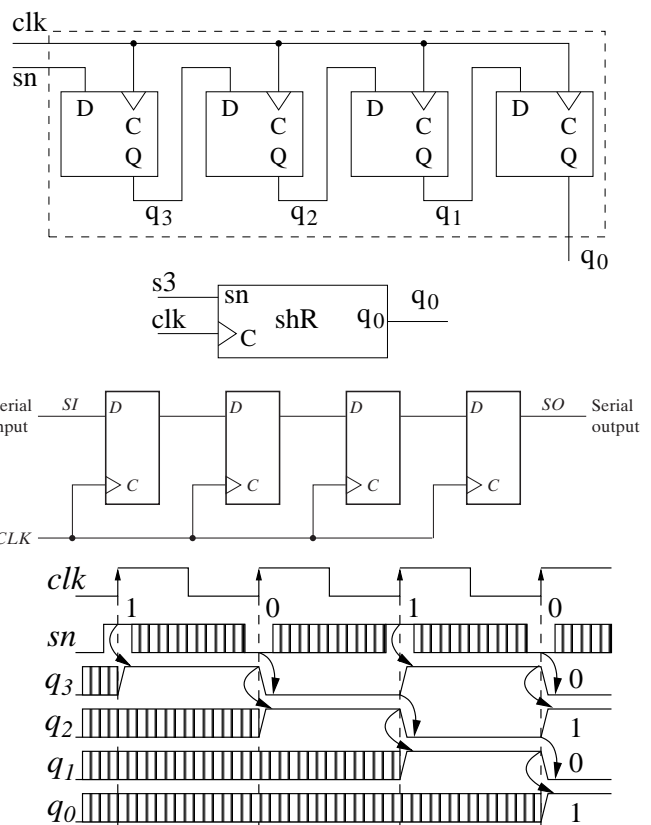- The timing diagram illustrate how a 4-bit binary word (0, 1, 0, 1) presented bit-by-bit at the serial input *sn* has been shifted into the register during the four consecutive rising edges of the clock.
- Such an operation can be referred to as a “serial load”.




 
### 10.1.3 A bi-directional shift register

- A bidirectional shift register can be considered as the most **typical sequential component**.
- The register performs both **shift-right** and **shift-left** operations and in addition **load** and **hold** operations.
- Operation to be performed is selected by a 2-bit opcode word.
- Note that we have three types of signals:
  - data (e.g. A, Q),
  - control signals, (Qop), and
  - a synchronizing (clocking) signal (clock).
- Specification of the register is given in the form of the following function table (4-bit structure is assumed):
- As usual, operations are performed on the rising edge of the clock.
- Note that there are two single-bit serial inputs, **sN** and **s0** from which the bits are shifted in on the vacated position during the respective shift operation.



Shift register, Q		
Qop	operation	
0	$Q \leftarrow Q$	hold
1	$Q \leftarrow (sN, Q[3:1])$	shiftR
2	$Q \leftarrow (Q[2:0], s0)$	shiftL
3	$Q \leftarrow A$	load

- The internal structure of the register consists of two main parts:
  - a set of  $N = 4$  edge-triggered D flip-flops with outputs **P** identical to the port signals **Q**, and inputs, **Din**.
  - The flip-flops ensure the positive-edge sensitivity,
  - a 4-bit 4-to-1 input multiplexer which effectively implements operations as specified in the function table, selecting appropriate signals to be loaded into the flip-flops.
- Timing diagram:

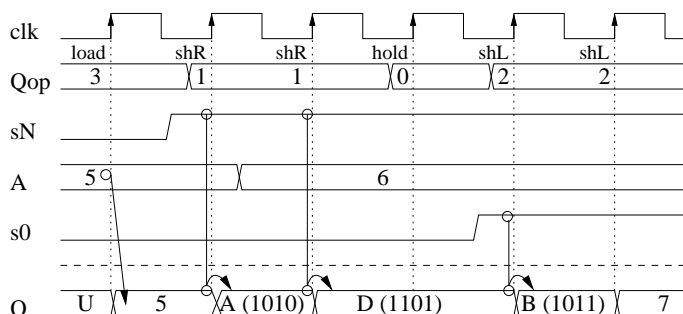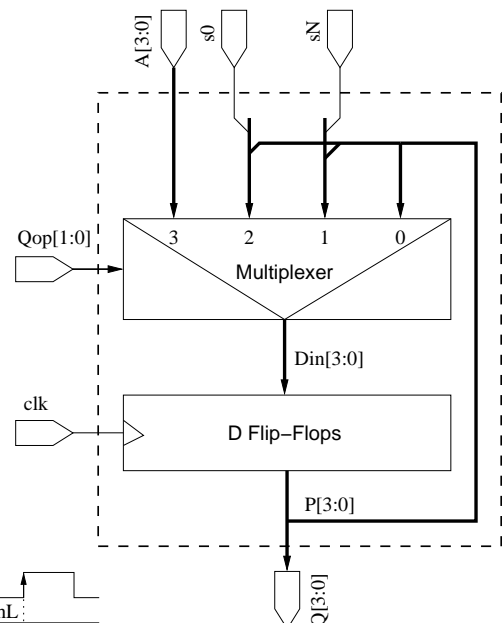

- VHDL code follows from the specification given in the block-diagram and the operation table.
- Two version of the code differs in the way the multiplexer is specified.

```

LIBRARY ieee;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all;
ENTITY shreg IS
    GENERIC ( N : integer := 4 ; M : integer := 2 ) ;
    PORT ( clk, sN, s0 : IN std_logic ;
          Qop : IN std_logic_vector(M-1 downto 0) ;
          A : IN std_logic_vector(N-1 downto 0) ;
          Q : OUT std_logic_vector(N-1 downto 0) ) ;
END shreg ;

ARCHITECTURE rtlA OF shreg IS
    SIGNAL P, Din : std_logic_vector(A'RANGE) ;
    CONSTANT nop : std_logic_vector(Qop'RANGE) := "00" ;
    CONSTANT shr : std_logic_vector(Qop'RANGE) := "01" ;
    CONSTANT shl : std_logic_vector(Qop'RANGE) := "10" ;
    CONSTANT ldd : std_logic_vector(Qop'RANGE) := "11" ;
BEGIN
    --- Qop range must be static eg. (1 downto 0)
    WITH Qop SELECT
        Din <= P
            WHEN nop ,
            sN & P(P'LEFT downto 1) WHEN shr ,
            P(P'LEFT-1 downto 0) & s0 WHEN shl ,
            A WHEN OTHERS ;

    -- flip-flop process
    PROCESS (clk)
    BEGIN
        IF clk'EVENT AND clk='1' THEN
            P <= Din ;
        END IF ;
    END PROCESS ;
    Q <= P ;
END rtlA ;

ARCHITECTURE rtlB OF shreg IS
    SIGNAL P, Din : std_logic_vector(A'RANGE) ;
    TYPE arrvec IS ARRAY (natural range <>)
        OF std_logic_vector(A'RANGE) ;
    SIGNAL YMUX : arrvec(0 to 2**M-1) ;
BEGIN
    YMUX <= ( P,
              sN & P(P'LEFT downto 1),
              P(P'LEFT-1 downto 0) & s0,
              A );
    Din <= YMUX(conv_integer(unsigned(Qop))) ;

```

- Both codes are similar and consists of three concurrent statements: one for a multiplexer, one for flip-flops  $P$  and the one which assigns internal signal  $P$  to an output port signal  $Q$ .
- In the **rtlA** architecture we have specified mnemonic names of constants, which increases code readability.
- The selected signal assignment expression is a bit more limited because the select signal size must be static.
- In the **rtlB** architecture, the multiplexer is specified as an array (table) of  $2^m$   $n$ -bit words.
- The words in the array are equivalent to the multiplexer inputs.
- The opcode  $Qop$  selects the  $n$ -bit word from the array

Figure 6-4: Serial Transfer from Register A to Register B from Mano

Consider bi-directional serial transfer of data


Discuss tri-state line driver.

10.2 Counters

- Counters are sequential circuits that increment or decrement a binary number stored in the flip-flops in response to the rising edge of the clock.
- The name counter is used rather than incrementer/decrementer because in the first application of the counters was counting the number of pulses coming to its clock input.

 
10.2.1 A ripple counter

- The simplest counter, known as a ripple counter, is build from simplified T flip-flops having only the clock input, that is, the toggle input is always on,  $T = 1$ .





- Note that the flip-flops toggle on the falling edge of the clock.
- In addition the reset signal  $rst$  sets the initial stage of the flip-flops to  $q = (0000)$
- Timing diagram demonstrate the delay problem associated with the ripple counter.

 The change of the states does not occur strictly on the clock edge, but there is a growing delay between stages.


  
### 10.2.2 Synchronous counter


- The basic synchronous counter is an improvement on the ripple counter and is typically build from the standard T flip-flops
- The  $q_i$  flip-flop is toggled only when the previous flip-flop  $q_{i-1} = 1$
- All flip-flops toggle synchronously on the rising edge of the clock.
- Timing diagram:



- There are three feature that can be added to the above counter:
  - We might want to start counting from a set number rather than from zero
  - A signal that indicates that the final stage  $q = 2^n - 1$  has been reached.
  - We might want to count both up and down.

 
### 10.2.3 Universal up-down counter

- The universal up-down counter performs four operations **hold**, **load**, **count up** (increment) and **count down** (decrement)
- Operations are selected by a 2-bit opcode word  $op[1:0]$ .
- In addition a signal  $cr$  indicated the maximum (all ones) or minimum (all zeroes) counter contents depending on the direction of counting.
- The above description is formalized by the following operation table:
- As usual, operations ar performed on the rising edge of the clock.
- For the hold and load operations  $cr$  has a “don’t care” value.



Up-down counter Q			
op	operation		cr
0	$Q \leftarrow Q$	hold	—
1	$Q \leftarrow A$	load	—
2	$Q \leftarrow Q + 1$	inc	$Q = \max$
3	$Q \leftarrow Q - 1$	dcr	$Q = \min$

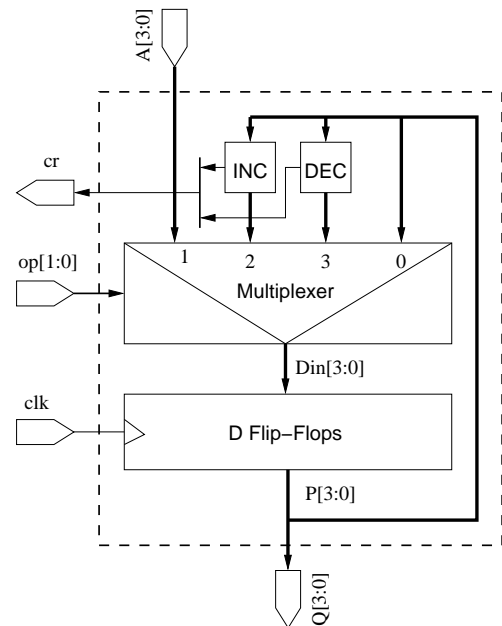- Such a universal counter is implemented using D flip-flops to store data and an appropriate excitation circuit.
- The first implementation of the excitation circuit can consist of a 4-to-1  $n$ -bit multiplexer preceded by combinational incrementer and decremter.



- A possible VHDL description closely follows the block diagram
- In order to be able to use a simple arithmetic statements to describe increment/decrement operations, the relevant signals are specified as being of the unsigned type
- For the unsigned signals we can write statements like

$$Y \leq P \pm 1$$

- Implementation of the multiplexer is identical to that discussed for the universal shift register.
- Note that the architecture `rtl_a` does not specify details of the implementation of the increment/decrement circuits leaving these details to the synthesizer to decide.

```


--          app, up-down counter
LIBRARY ieee;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all;
ENTITY udCnt IS
  GENERIC ( N : integer := 4 ; M : integer := 2 ) ;
  PORT ( clk : IN std_logic ;
        op : IN std_logic_vector(M-1 downto 0) ;
        A : IN std_logic_vector(N-1 downto 0) ;
        Q : OUT std_logic_vector(N-1 downto 0) ;
        cr : OUT std_logic ) ;
END udCnt ;
ARCHITECTURE rtl_a OF udCnt IS
  SIGNAL AA, P, Din : unsigned(A'RANGE) ;
  TYPE arrvec IS ARRAY (natural range <>)
    OF unsigned(A'RANGE) ;
  SIGNAL YMUX : arrvec(0 to 2**M-1) ;
BEGIN
  AA <= unsigned(A) ;
  YMUX <= (P, AA, P + 1, P - 1) ; -- multiplexer
  Din <= YMUX(conv_integer(unsigned(op))) ;
  cr <= '1' WHEN ((op(0) = '0') AND (P = 2**N-1))
    OR ((op(0) = '1') AND (P = 0))
    ELSE '0' ;

  -- flip-flop process
  PROCESS
  BEGIN
    WAIT UNTIL clk'EVENT AND clk='1' ;
    P <= Din ;
  END PROCESS ;

  Q <= std_logic_vector(P) ;
END rtl_a ;

```

 - Simulation waveforms for the universal up-down counter are shown below:



- Inspect the waveforms and verify that all operations are performed as specified in the counter operation table.

- In this architecture of the up-down counter we specify details of implementation of the incrementer/decrementer circuit.
- Following considerations from sec. 7.2 we observe that input and output signals of the incrementer and decrementer are related through the following arithmetic equalities:

$$\text{Incrementer: } c + p = 2 \cdot d + y$$


$$\text{Decrementer: } -c + p = -2 \cdot d + y$$

- If we denote by  $dn$  a signal to count down, then the arithmetic equalities result in the following logic equations:

$$y = p \oplus c$$

$$d = c \cdot (dn \oplus p)$$

 - The 1-bit increment/decrement component can be now connected into an  $n$ -bit component as discussed in sec. 7.2.
- The initial carry  $c_0$  must be set up to 1 for increment and to 0 for decrement operation. Otherwise the output will be equal to input.
- We can use this property to implement the hold operation.






- If we use the following increment/decrement circuit, the excitation circuits for the universal up-down counter can be much simplified:
- From the following truth table we can specify the required control signals:

op	op <sub>1</sub>	op <sub>0</sub>	cd	c <sub>0</sub>
hold	0	0	0	0
load	0	1	–	–
inc	1	0	0	1
dec	1	1	1	0

$$cd = op_0$$

$$c_0 = op_1 \cdot \overline{op_0}$$

$$ld = \overline{op_1} \cdot op_0$$

 

- The modified VHDL architecture can be written in the following way (D flip-flops has been omitted):

```

ARCHITECTURE rtlb OF udCnt IS
    SIGNAL P, Y, Din : std_logic_vector(A'RANGE) ;
    SIGNAL          c : std_logic_vector(N downto 0) ;
BEGIN
    c(0) <= op(1) ;

    gnrt: FOR i IN 0 TO N-1 GENERATE -- INC/DEC
        Y(i) <= P(i) XOR c(i) ;
        c(i+1) <= c(i) AND (op(0) XOR P(i)) ;
    END GENERATE gnrt ;

    cr <= c(N) ;
    Din <= A WHEN op = "01" ELSE Y ;

    -- flip-flop process

END rtlb ;

```