

11 Synchronous State Machines

- Synchronous (finite) state machines are also known as clocked sequential circuits.
- Registers and counters are examples of specialised synchronous sequential circuits.
- Recall that in a general case we have two types of state machines, Mealy and Moore, that differ in the way the output signals are form.


state equations: $Q(t + 1) = f(Q(t), X(t))$

D FFs excitation eqs: $D(t) = f(Q(t), X(t))$

Output equations:

Mealy: $Y(t) = g(Q(t), X(t))$


Moore: $Y(t) = g(Q(t))$

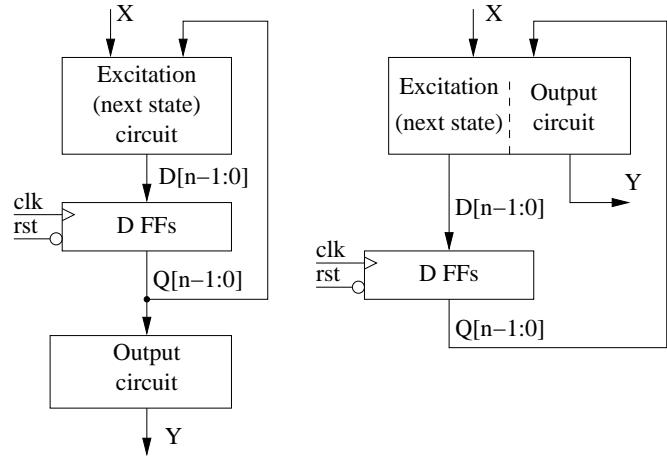

- In the Moore state machine the output signals are re-coded state signals.
- In the Mealy state machine the output signals depends both on state signals and input signals.
- Typically, state machines are primarily described by **state diagrams**.
- State diagrams are converted into **state and output tables** from which the structure of the excitation and output circuits can be derived.

 11.1 Example of a Moore state machine


- Consider a Moore state machine described by the following symbolic state diagram:
- The state machine has a single input, x , three states labeled a, b, c and a single binary output $y \in \{ya, yb\}$
- At least two state signals, say q_1, q_0 are required to code three states.
- Unlike in the asynchronous case, the states can be flexibly coded, simplicity of the excitation circuit being the only limitation.
- We start with **state assignment** replacing symbolic names of the states with their binary equivalent. This results in the following state state diagram:
- The state machine now has two D flip-flops q_1, q_0 .
- Note that in the synchronous case the machine is in any given state for at least one clock cycle.



- The next step is to convert the state diagram into the state and output equations.
- the excitation table for D flip-flops is identical with the state table.

| x | Q_1 | Q_0 | D_1 | D_0 |
|-----|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | — | — |
| 1 | 1 | 0 | — | — |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 |

| Q_1 | Q_0 | y |
|-------|-------|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | — |
| 1 | 1 | 1 |

 

- Resulting Karnaugh maps

| D_1 | $Q_1 Q_0$ | | | |
|-------|-----------|----|----|----|
| x | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 0 | — |
| 1 | 0 | 1 | 0 | — |

| D_0 | $Q_1 Q_0$ | | | |
|-------|-----------|----|----|----|
| x | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | — |
| 1 | 1 | 1 | 0 | — |

Excitation and output equations:

$$D_1 = x \cdot \bar{Q}_1 \cdot Q_0$$

$$D_0 = x \cdot \bar{Q}_1 + \bar{x} \cdot Q_1 = x \oplus Q_1$$

$$y = Q_0$$

- Excitation and output equations:



$$D_1 = x \cdot \bar{Q}_1 \cdot Q_0$$

$$D_0 = x \cdot \bar{Q}_1 + \bar{x} \cdot Q_1 = x \oplus Q_1$$

$$y = Q_0$$

- The excitation circuit generates input signals to the flip-flops
- These signals are clocked in during the rising edge of the clock.
- The output circuits is trivial in this example, but in general the output signals are generate by a combinational circuit from the state signals.
- Timing diagram:

Logic diagram:

 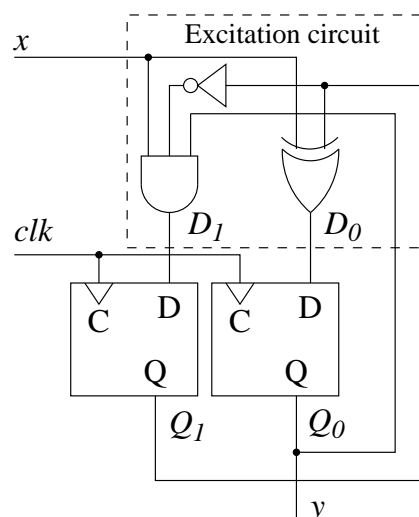

VHDL specification of the Moore state machine

```

library IEEE ;
use IEEE.std_logic_1164.all ;

ENTITY MSTM IS
  PORT ( x, clk : IN  STD_LOGIC ;
        Q : OUT  STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        y : OUT  STD_LOGIC
        ) ;
END MSTM ;

ARCHITECTURE behv OF MSTM IS

  -- TYPE states IS (sa, sb, sc) ;
  -- SIGNAL D : states := sa ;

  SIGNAL D, stt : STD_LOGIC_VECTOR(1 DOWNTO 0) ;
  -- a "hard" encoding of states:
  CONSTANT sa : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
  CONSTANT sb : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
  CONSTANT sc : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
  -- encoding of output signals
  CONSTANT ya : STD_LOGIC := '0' ;
  CONSTANT yb : STD_LOGIC := '1' ;

BEGIN
  -- to synthesize edge-triggered flip-flops
  clkd: PROCESS ( clk )
  BEGIN
    IF clk'EVENT AND clk = '1' THEN
      stt <= D ;
    END IF ;
  END PROCESS clkd ;

  -- the stm process describes the transitions between states -- and the output signals

```

A.P. Papliński

11-5

```

stm: PROCESS ( Q )
BEGIN
  -- default assignments
  D <= Q ;
  y <= ya ;

  CASE stt IS -- state transitions and output signals

  WHEN sa =>
    y <= ya ;
    IF x = '0' THEN
      D <= sa ; ELSE D <= sb ;
    END IF ;

  WHEN sb =>
    y <= yb ;

    CASE x IS
      WHEN '0' => D <= sa ;
      WHEN OTHERS => D <= sc ;
    END CASE ;

  WHEN OTHERS => --- when sc
    y <= yb ;

    CASE x IS
      WHEN '0' => D <= sb ;
      WHEN OTHERS => D <= sa ;
    END CASE ;

  END CASE ;
END PROCESS stm ;
Q <= stt ;
END behv ;


```

A.P. Papliński


11-6

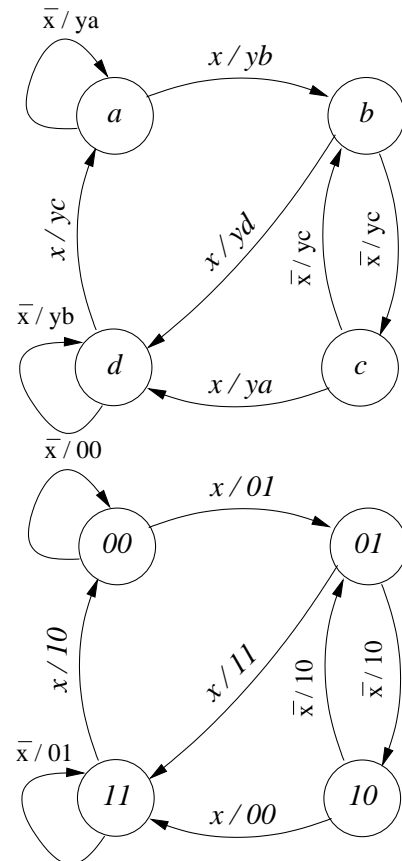11.2 Example of a Mealy state machine

- Consider a Mealy state machine described by the following symbolic state diagram:
- The state machine has
 - a single input, x ,
 - four states labeled a, b, c, d that will be coded using (at least) two state signals q_1, q_0 , and
 - binary output $y \in \{ya, yb, yc, yd\}$ that will be coded by two output signals y_1, y_0
- Note that the output signals depend now on both the state signals and the input signal(s).
- Labeling of the output signals might be confusing: it is the **state that arrow originates** from that generates the output signal together with the input signal.
- After **the state and output assignment** we have the following state state diagram:



- Timing diagram

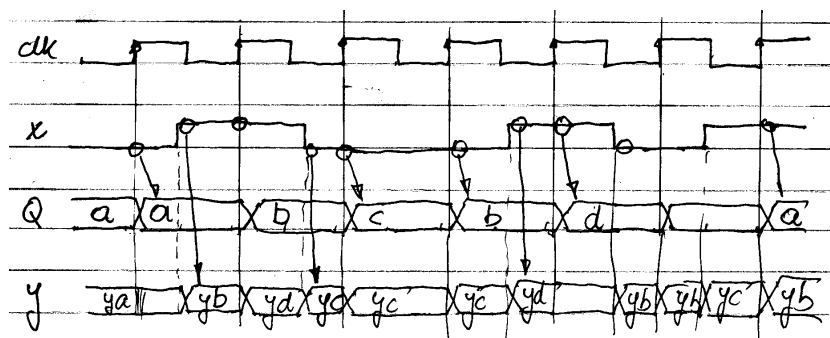


- Note that output signals change in response to a change in both input signals and state signals.
- The next step is to convert the state diagram into the state and output equations.
- the excitation table for D flip-flops is identical with the state table.

The excitation (state) and output tables:

| x | Q_1 | Q_0 | D_1 | D_0 |
|-----|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

| x | Q_1 | Q_0 | y_1 | y_0 |
|-----|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

 

Resulting Karnaugh maps:

| D_1^+ | Q_1Q_0 | | | |
|---------|----------|----|----|----|
| x | 00 | 01 | 11 | 10 |
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |


| D_0^+ | Q_1Q_0 | | | |
|---------|----------|----|----|----|
| x | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 |

| y_1^+ | Q_1Q_0 | | | |
|---------|----------|----|----|----|
| x | 00 | 01 | 11 | 10 |
| 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |

| y_0^+ | Q_1Q_0 | | | |
|---------|----------|----|----|----|
| SR | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 |

Write out the logic equations as an exercise.

Logic diagram:

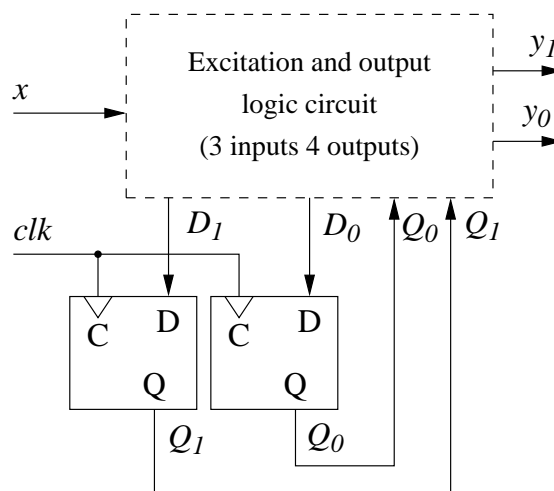

Write a VHDL description as an exercise