

## Practical 7: Asynchronous sequential circuits

---

### 7.1 About this practical

The objective of this practical is to design and test three implementations of a D flip-flop as an asynchronous sequential circuit.

### Contents

7.1	About this practical . . . . .	1
7.2	A two-state-signals implementation of a D flip flop . . . . .	1
7.3	A two-state-signals implementation of a D flip flop . . . . .	2
7.4	A three-state-signals implementation of a D flip flop . . . . .	4
7.5	The report . . . . .	5

### 7.2 A two-state-signals implementation of a D flip flop


The first implementation is based on the generic description of a D flip-flop in VHDL which is based on the **process** statement and the **event** attribute.

- Start the Design manager and create a new project: **P7you**
- Create a VHDL design view with the
  - Entity name: **DFFyou**
  - Architecture name: e.g., **ahdl**
- In the **VHDL editor window** enter an appropriate entity specification for the D flip-flop and
- the architecture to be as follows (watch the single quotes!)

```


ARCHITECTURE ahdl OF DFFyou IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clk'EVENT AND clk = '1') THEN
      Q <= D ;
    END IF ;
  END PROCESS ;
END ARCHITECTURE ahdl;
```

- Save the VHDL file.
- Compile the VHDL specification selecting in the VHDL editor window:  
Tasks → ModelSim flow → Run single
- At the conclusion of the successful compilation a window **Start ModelSim** appears. If you accept its default settings, it will open ModelSim simulation window.
- Write and execute an appropriate simulation script to generate waveforms conceptually similar to the following:

 

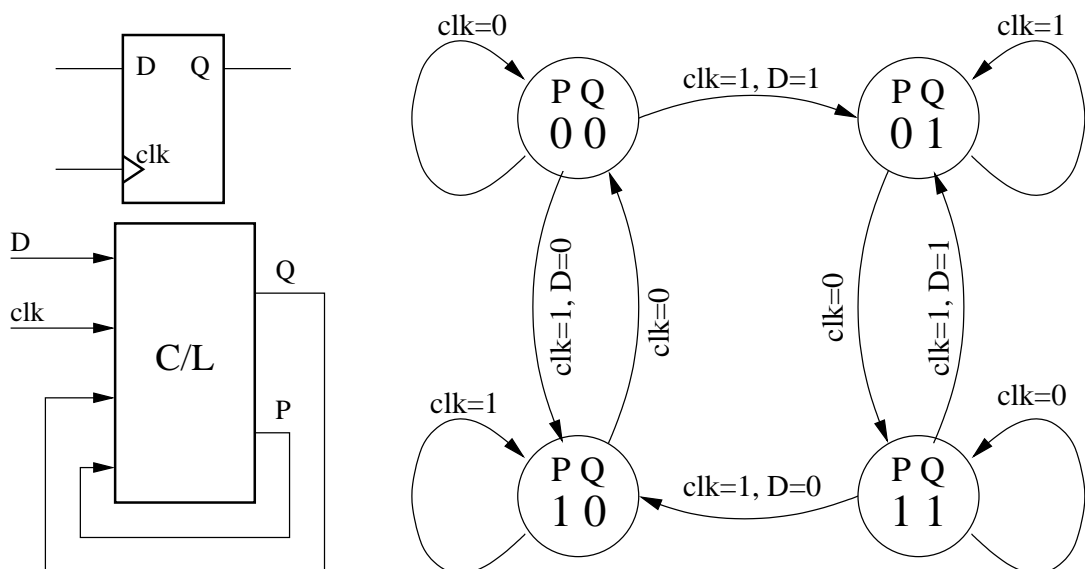
### 7.3 A two-state-signals implementation of a D flip flop

- In the second implementation of the D flip-flop we start with the state diagram with two state signals  $P$  and  $Q$  as discussed in the lecture notes:



 - Subsequently, we convert the **state diagram** into the **state transition** table.




clk	D	P	Q	P+	Q+
0	-	0	0	0	0
1	0	0	0	1	0
1	1	0	0	0	1
0	-	0	1	1	1
1	-	0	1	0	1
0	-	1	0	0	0
1	-	1	0	1	0
0	-	1	1	1	1
1	0	1	1	1	0
1	1	1	1	0	1

- Create a new VHDL architecture flowing from the above state table similar to the following:

```


ARCHITECTURE ttbl OF DFFyou IS
  TYPE arr2d IS ARRAY (natural range <>,
                       natural range <>) OF std_logic;
  CONSTANT ttDff : arr2d(1 to 2, 0 to 15) := (
    -- truth table for P+ Q+
    --0123456789abcdef (P, Q, clk, D)
    "00101110000111110" , --1 P
    "00011111100001101" ); --2 Q
  SIGNAL P, QQ : std_logic ;
  SIGNAL S : std_logic_vector (3 downto 0) ;
  SIGNAL Si : integer range 0 to 15 ;
BEGIN
  S <= (P, QQ, clk, D) ;
  Si <= conv_integer(unsigned(S)) ;
  -- reading from the truth table
  P <= ttDff (1, Si) ;
  QQ <= ttDff (2, Si) ;
  Q <= QQ ;
END ttbl ;
  
```

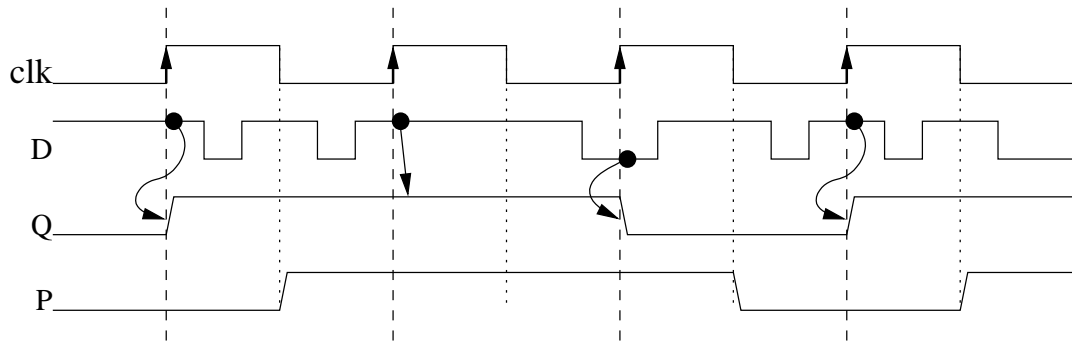- Simulate the VHDL design to obtain waveforms similar to the following:


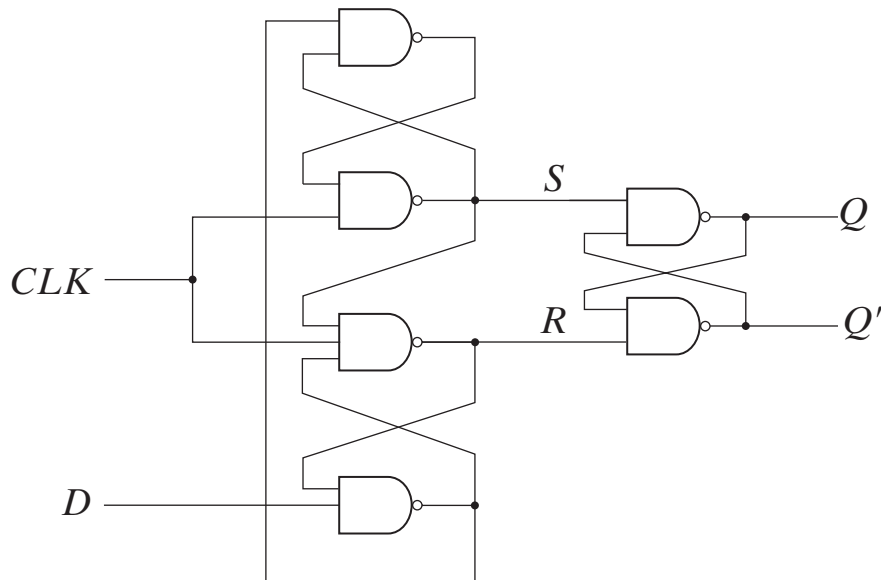
### 7.4 A three-state-signals implementation of a D flip flop

- The third implementation of the D flip-flop is based on the following NAND-based logic diagram.



- Use the **graphical entry** to specify the D flip-flop given by the above logic diagram.
- Simulate the design using an appropriate simulation script. Show the internal *R* and *S* signals.

## 7.5 The report

In your report (due after prac 8) include the results in the form of:

- Relevant state diagrams, state tables, state equations, other logic equations,
- block/logic diagrams,
- VHDL programs,
- simulation scripts,
- simulation waveforms,
- **short** description of the above.

Wherever possible publish the results selecting in the **Block Diagram** window

**File** → **HTML Export ...** . Specify the export target directory to be `... \DigDes \Reports`.